



(Following Paper ID and Roll No. to be filled in your Answer Book)

**PAPER ID : 131305**

Roll No.

--	--	--	--	--	--	--	--	--	--

### B. Tech.

(SEM. III) (ODD SEM.) THEORY  
EXAMINATION, 2014-15  
DIGITAL ELECTRONICS

Time : 3 Hours]

[Total Marks : 100

**Note :** Attempt ALL questions.

**1** Answer any **four** parts : **5×4=20**

- (a) Represent the decimal number 6208 (i) in 2,4,2,1 code, (ii) in BCD and (iii) as a binary number.
- (b) Define parity codes. Design odd parity generator and parity checker for three bit codes data.
- (c) Construct  $16 \times 1$  Multiplexer with the help of  $4 \times 1$  Multiplexer.
- (d) Compute M-N and N-M using 1's compliment and 2's compliment methods. Where, M=110100 and N=10101.
- (e) Implement Boolean function of Ex-NOR with the help of (i) using NAND Gates only and (ii) using NOR Gates only.
- (f) Simplify using Karnaugh map the following Boolean Function

$$F(w,x,y,z) = \sum (1,5,7,10,15)$$


$$D(w,x,y,z) = \sum (3,2,6)$$

2 Answer any **four** parts : **5×4=20**

- (a) Implement a full subtractor with two half subtractors.
- (b) Design and explain the logic and circuit of 4 bit magnitude comparator.
- (c) Design and explain the logic and circuit of 4-bit by 3-bit binary multiplier.
- (d) Construct a 5×32 decoder with 3×8 decoders and 2×4 decoder.
- (e) Implement the following Boolean function with the help of 4×1 multiplexer  
 $F(x,y,z) = \sum (1,2,6,7)$
- (f) Design and explain the logic and circuit of BCD Adder.

3 Answer any **two** parts : **10×2=20**

 - (a) Design a modulo-14 ripple counter. Give its waveforms displaying output states.
- (b) Design a synchronous counter using JK Flip Flop which can count the following cycle. Also draw the bush diagram.



- (c) (i) Draw and explain the circuit of bidirectional shift register with parallel load.
- (ii) Draw and explain the circuit of Ring Counter and Johnson Counter. Write the output states of these counters.

4 Answer any **two** parts : **10×2=20**

- (a) Draw and explain the circuit of a memory binary cell. Using this binary cell draw and explain the circuit of 8×5 RAM.
- (b) Explain PROM, PLA and PAL. Implement the following Boolean functions with a PLA.  $F_1(x,y,z) = \sum (0,2,3,4)$  ;

$$F_2(x,y,z) = \sum (2,4,6,7)$$

- (c) Explain ASM Chart. Describe the ASM chart and control logic of Binary Multiplier.

5 Answer any **two** parts : **10×2=20**

- (a) An asynchronous sequential circuit is described the excitation and output functions as given below.  
 $Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$  ;  $Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$  ;  $z = x_2 + y_1$   
 (i) Draw the logic diagram of the circuit (ii) Derive the transition and output map (iii) Obtain a flow table of the circuit.
- (b) Analyze SR latch with NOR gates. The Boolean functions for the inputs of an SR latch are  
 $S = x_1'x_2'x_3 + x_1x_2x_3$   
 $R = x_1x_2' + x_2x_3'$   
 Obtain the circuit diagram using a minimum number of NAND Gates.
- (c) Obtain a binary state assignment for the reduced flow table shown below. Avoid critical race conditions. Also obtain the logic diagram of the circuit using NAND latches and gates.

		$x_1x_2$			
		00	01	11	10
a	a	(a), 0	(a), 1	b, -	d, -
	b	a, -	(b), 0	(b), 0	c, -
	c	a, -	- , -	d, -	(c), 0
	d	a, -	a, -	(d), 1	(d), 1