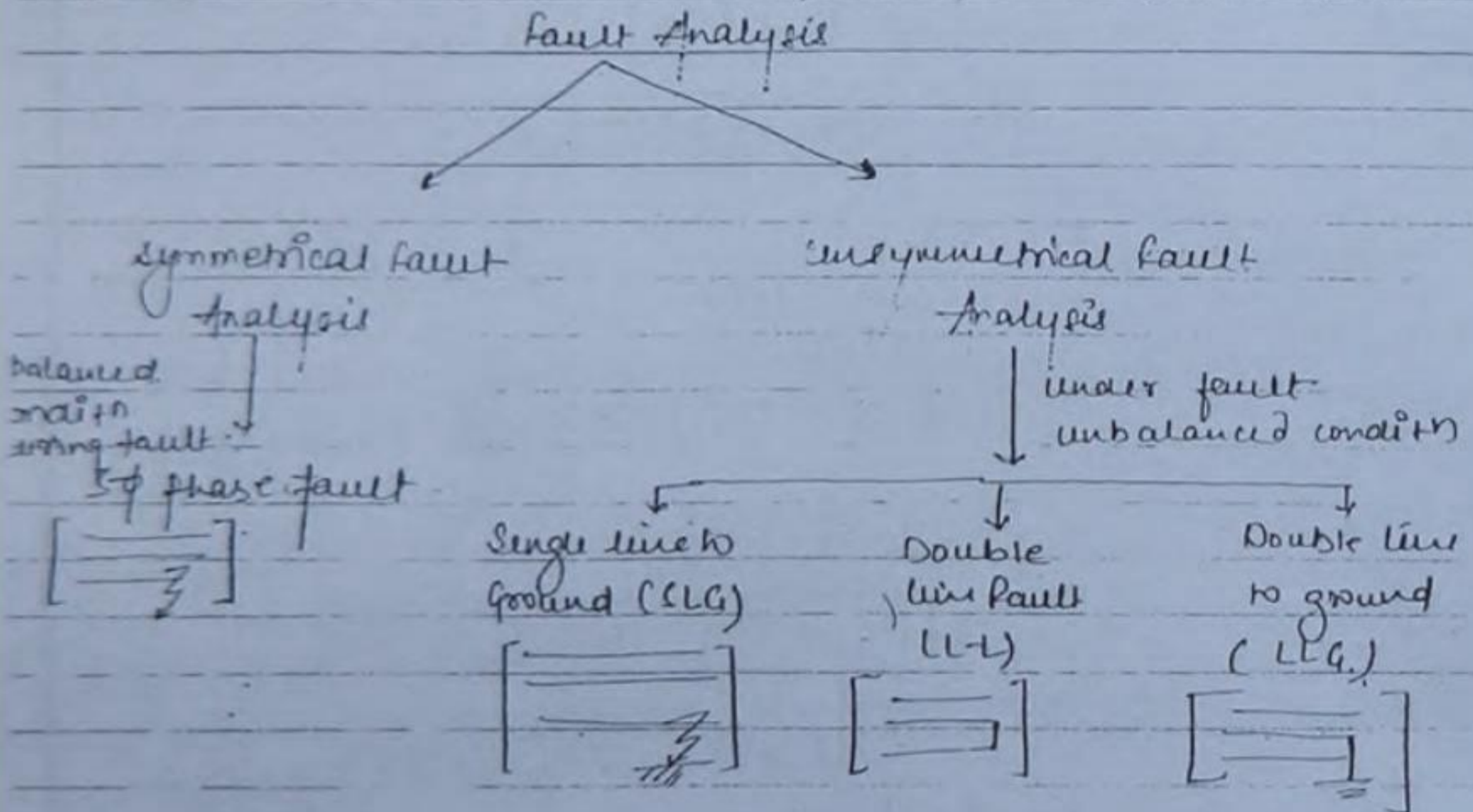


FAULT ANALYSIS

→ Main purpose of fault analysis is design circuit breaker. (switch gear)

$I_f \rightarrow$ Fault current

$I_f \times V_f =$ Fault MVA (Circuit Breaker rating).



• Most severe fault is 3φ fault and least is SLG.

• During design of circuit breaker, 3φ fault is counted.

• SLG fault is used in relay design. (proper setting)

• The unsymmetrical fault analysis is also an important

→ Single line diagram: - indicates that original P.S is 3 ϕ and working at "balanced condition".

study since coz the knowledge of all types of fault is important to provide proper setting for the relay.

PER UNIT Analysis: -
Per unit value is unitless value.

$$\text{P.U. value} = \frac{\text{Actual value in some unit}}{\text{Base/reference value in same unit}}$$

Advantage of P.U Method: -

- It simplifies power sys calculation.
- It avoids the discontinuity problem posed by presence of XMR in power system n/w. (Chief advantage)

* Single line diagram:

Y
B

$$I_n = I_r + I_r + I_b = 0$$

$$V_n = I_n Z_n = 0$$

$$S_n = -V_n I_n^* = 0$$

no imaginary power
neutral of

Single line diagram is called as zero power bus

finally we have




* Single line diagram: the single line diagram represents of

* circuit breaker rating should be high

power system indicates that original per system is 3ϕ and its working under balanced condition. When 3ϕ work under balanced condition, the advantage is by working on single phase basis (by applying p.u. method), we can claim that we have completed 3ϕ analysis.

Explanation of point (3):-

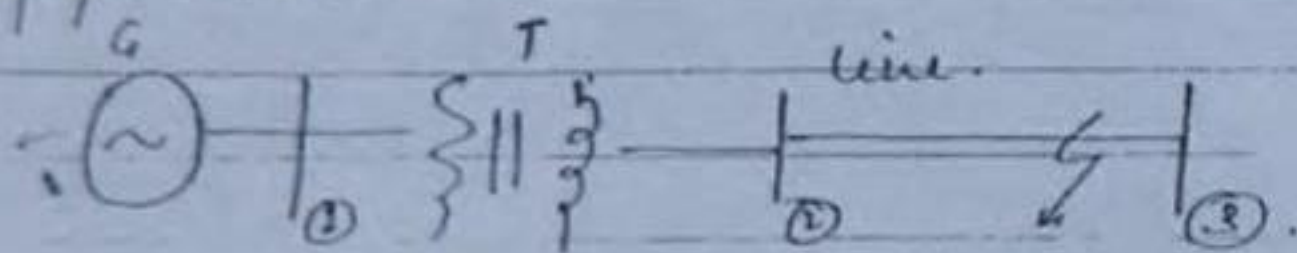

Assumption for short circuit calculation:

- ① Capacitance of circuit neglected (MVA \rightarrow KV)
- ② resistance of ~~total~~ ^{individual equipment} neglected.

Note: By neglecting the resistance and capacitance the only parameter which limit s.c. current is the inductance.*
* Fault current is inductive, lagging current, lagging reactive power. Fault demands \uparrow lagging reactive power.

* whenever fault occurs, the voltage of other phase decreases due to armature reaction (demagnetization - low magnetic field).


* Fault current is max^m in subtransient state as minimum reactance.

③ Effect of saliency (salient pole) is neglected; the

effect of non-uniform air of salient pole is neglected.

* During S.C the voltage is effected, frequency constant (Active power not change whereas reactive).

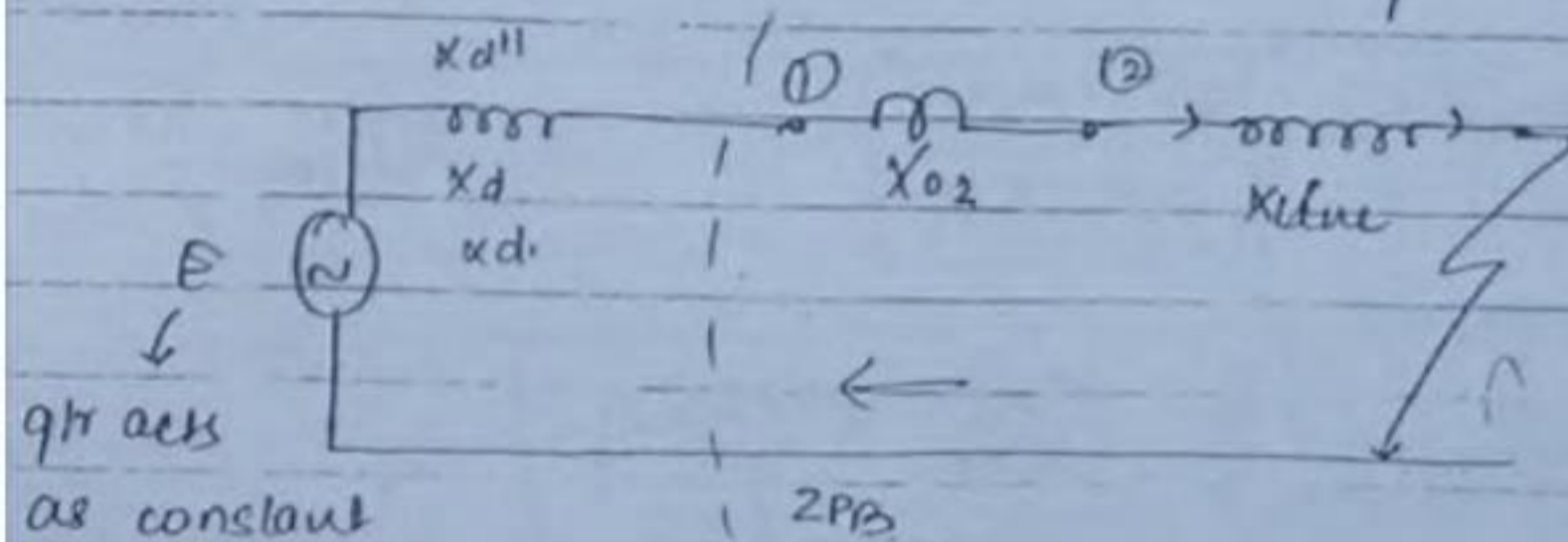
* In load analysis the frequency prominently changes



q/r axis
as constant
voltage
source

(low voltage) side (High voltage side)

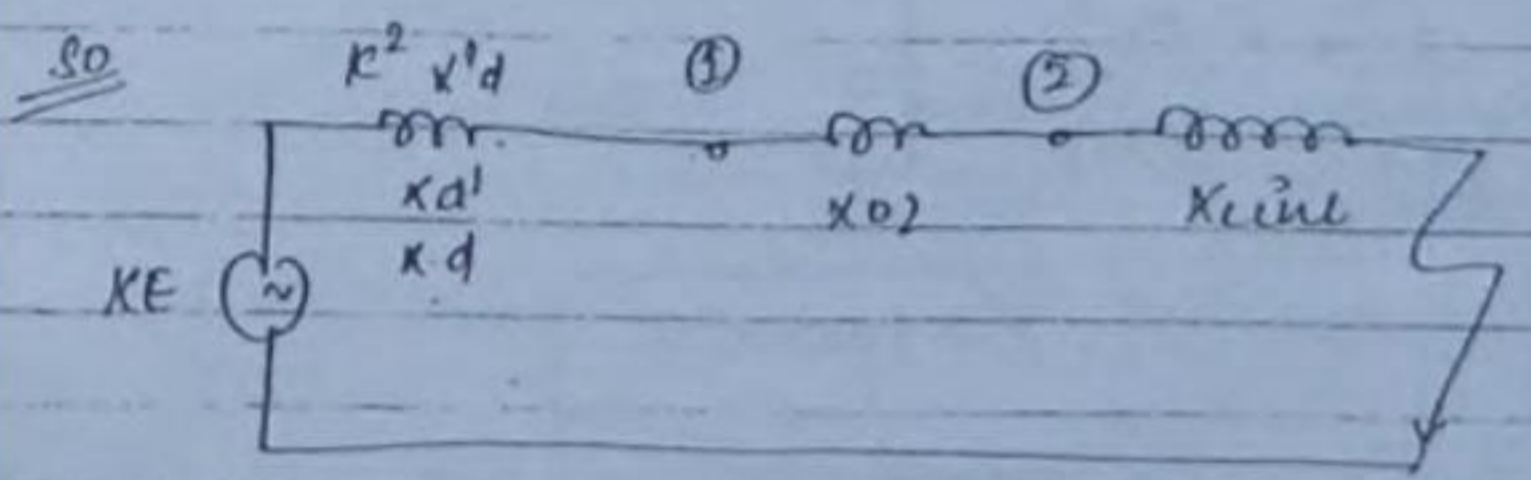→ X_{int} can be represented as:
 X_{01} primary
 X_{02} secondary



converting q/r to high voltage side (k → turn ratio)

this method is practically impossible. so pu method is used.

- $Z_{eq}(LV) \neq Z_{eq}(HV)$
- $Z_{eq}(LV(pu)) = Z_{eq}(HV(pu))$

In pu method - X_{int} are represented as the series reactance and discontinuity is removed as the value of impedance, current remain same at both ends LV-HV

Selection of base values: (only 4 P, V, I, Z)

③ We select base values for Power and voltage.

→ Base voltage: $-KV_b$.

Base voltage = 100 kV

→ Base power: KVA_b or MVA_b .

Base power = 200 MVA

→ Base current in (Ampere) =

$$I_b = \frac{KVA_b}{KV_b}$$

$$\frac{200}{100} = 2 \times 1000$$
$$= 2000 A$$

$$I_b = \frac{MVA_b \cdot 1000}{KV_b} A$$

acts as
conversion
factor

→ Base impedance (in Ω) =

$$Z_b = \frac{KV_b^2}{MVA_b} \Omega$$

objective

$$Z_b = \frac{KV_b^2}{KVA} \times 1000 = \Omega$$

conversion
factor

include

→ Base values considered when for calculation of 3 ϕ .

→ 3 ϕ power, line voltage.

$$Z_{b,1\phi} = \frac{KV_{b,1\phi}^2}{MVA_{b,1\phi}}$$

$$Z_{b,3\phi} = \frac{KV_{b,3\phi}^2}{MVA_{b,3\phi}}$$

$$\Rightarrow \left(\sqrt{3} \times KV_{b,1\phi} \right)^2 = \frac{K^2 V_{b,1\phi}}{3 \times MVA_{b,3\phi}} = \frac{K^2 V_{b,1\phi}}{MVA_{1\phi}}$$

$$Z_{b,3\phi} = Z_{b,1\phi}$$


② whenever we change base values, pu value change not actual values.

$$Z_{pu,old} = \frac{Z_{actual}}{Z_{b,old}} = \frac{Z_{actual}}{KV_{b,old}^2 / MVA_{b,old}}$$

$$Z_{pu,new} = \frac{Z_{actual}}{Z_{b,new}} = \frac{Z_{actual}}{KV_{b,new}^2 / MVA_{b,new}}$$

$$Z_{pu,new} = Z_{pu,old} \times \left(\frac{KV_{b,old}}{KV_{b,new}} \right)^2 \times \left(\frac{MVA_{b,new}}{MVA_{b,old}} \right)$$

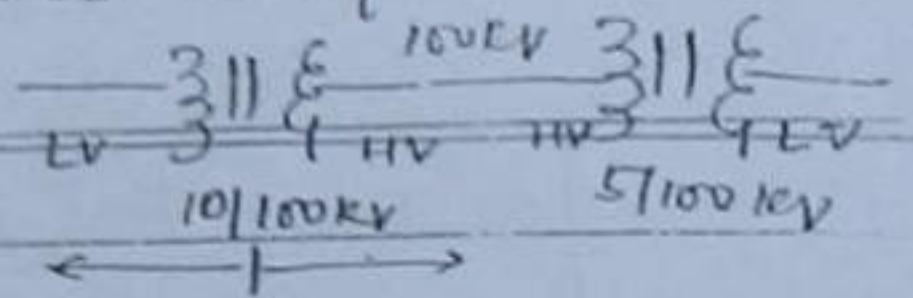→ If two π ms are connected in series no of base values is 3
 One common, LVT_1 , $HV(T_1, T_2)$, LVT_2



Example:

Q) An equipment is having 10 pu impedance on 100 MVA, 10KV. Its pu impedance on 10 MVA, 100KV is —

$$Z_{pu-nw} = 10 \times \left(\frac{10}{100}\right)^2 \times \left(\frac{10}{100}\right)$$


$$10 \times \frac{100}{10000} \times \frac{10}{100}$$

$$= 0.01 \text{ pu}$$

Rules of selecting base values when π ms is present in n/w:

1) In circuit containing π ms, we have to select two set of base values one for LV and another for HV side.

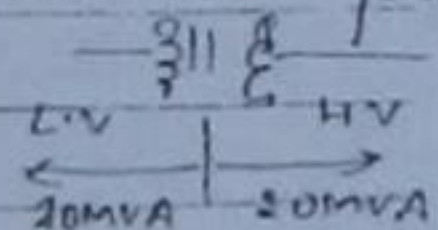
2) Common base power is selected for both sets or for entire n/w.



3) Two different base voltages must be selected for LV and HV in such a way their ratio must be equal to transformation ratio of original π ms.

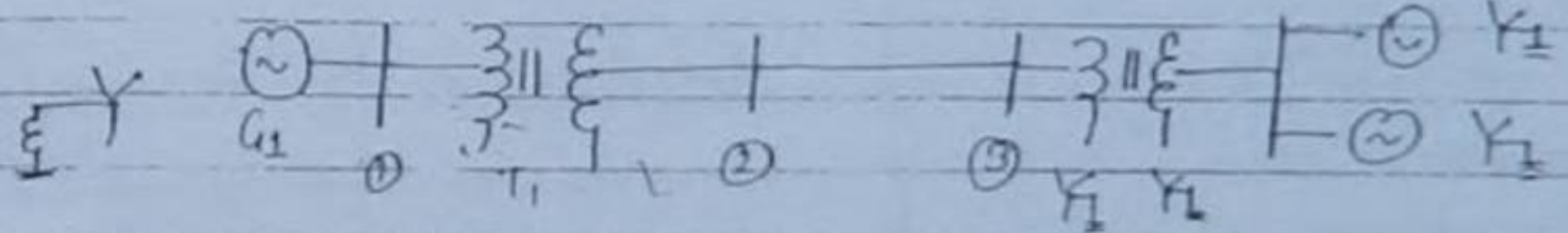Example:-

Obtain the pu equivalent reactance diagram for the power s/m shown below



G1: 30 MVA, 10.5 KV, $x''_d = 1.6 \text{ pu}$

G2: 15 MVA, 6.6 KV, $x''_d = 1.2 \text{ pu}$

G3: 25 MVA, 6.6 KV, $x''_d = 0.56$

T1 = 15 MVA, 33/10.5 KV, $X = 15.2 \Omega$
p pu on HV

T2 = 15 MVA, 33/6.6 KV, $X = 16 \Omega$ / pu
on HV side

T.L = 20.5Ω / pu

Initial values (reactance)	LV side of T1	HV side of T1 and T2	LV side of T2
G1	1.6 pu on 30 MVA, 10.5 KV	—	—
G2	—	—	1.2 pu on 15 MVA, 6.6 KV
G3	$15.2 \times \frac{11}{33} = 1.6 \text{ pu}$	15.2 pu	0.56 pu on 25 MVA, 6.6 KV
T1	—	—	—
T2	—	16 Ω / pu	0.66 Ω / pu
L	—	20.5 Ω / pu	—

Base value =

	LV side of T ₁	HV side of T ₁ /T ₂	LV side of T ₂
MVA _b	30 MVA	30 MVA	30 MVA
KV _b	11 KV	33 KV	6.2 KV
Z _b	$\frac{11^2}{30} = 4.03 \Omega$	$\frac{33^2}{30} = 36.3 \Omega$	$\frac{6.2^2}{30} = 1.28 \Omega$

formula used = $\frac{KV_b^2}{MVA_b}$

G1: 1.6 pu on 30 MVA, 10.5 KV

$$Z_{pu \text{ new}} = 1.6 \times \left(\frac{30}{30}\right) \times \left(\frac{10.5}{11}\right)^2$$

$$Z_{pu \text{ new}} = 1.46 \text{ pu}$$

$$V_{G1} = \frac{10.5}{11} = 0.96 \text{ pu}$$

Actual
Base

G2: 1.2 pu on 15 MVA, 6.6 KV

$$Z_{pu \text{ new}} = 1.2 \times \left(\frac{30}{15}\right) \times \left(\frac{6.6}{6.2}\right)^2$$

$$= \boxed{Z_{pu(new)} = 2.72 \text{ pu}}$$

$$V_{G2} = \frac{6.6}{6.2} = 1.06 \text{ pu} \quad \boxed{V_{G2} = 1.06 \text{ pu}}$$

G3: 0.56 pu on 2.5 MVA 6.6 kV

$$Z_{pu(new)} = 0.56 \times \left(\frac{30}{2.5}\right) \times \left(\frac{6.6}{6.2}\right)^2$$

$$\boxed{Z_{pu(new)} = 0.76 \text{ pu}}$$

$$V_{G3} = \frac{6.6}{6.2} = 1.06 \text{ pu}$$

T1: 1.69 pu w.r.t LV side
base impedance on LV side of T1 = 4.03 Ω

$$X_{T.p.u.} = \frac{1.69 \Omega}{4.03 \Omega} = 0.41 \text{ pu}$$

1.52 pu w.r.t HV side

base impedance = 36.33 Ω ✓

$$X_{T.p.u.} = \frac{1.52}{36.33} = 0.41 \text{ pu}$$

$$\boxed{X_{T.p.u.} = 0.41 \text{ pu}}$$

T2

0.56 pu w.r.t 1.28 LV side of T2

base impedance on LV side of T2 = 1.28 Ω

$$X_{T.p.u.} = \frac{0.56}{1.28} = 0.4375 \text{ pu}$$

16 MVA w.r.t to HV side of T2

Base value = 36.33Ω

$$X_{T2} = \frac{16}{36.33} = 0.434 \text{ p.u.}$$

Line


$$X_{T2} = 0.434 \text{ p.u.}$$

$X_L = 20.5$ on HV side T2 and T1

base value = 36.33Ω


$$X_{line} = \frac{20.5}{36.33} = 0.56 \text{ p.u.}$$

$$X_{line} = 0.56 \text{ p.u.}$$

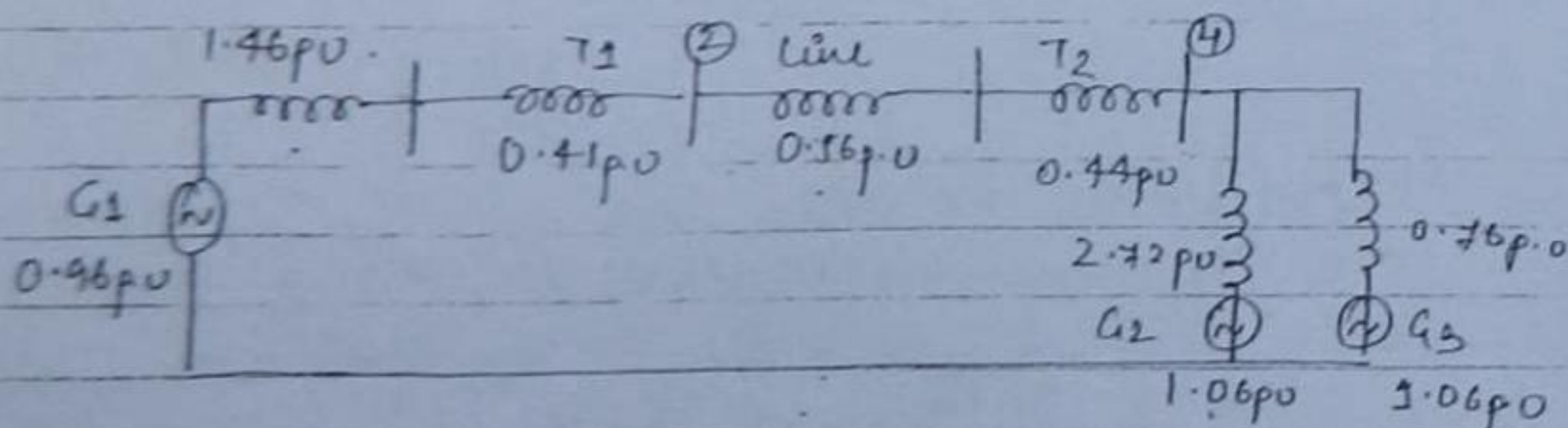

Per unit reactance diagram

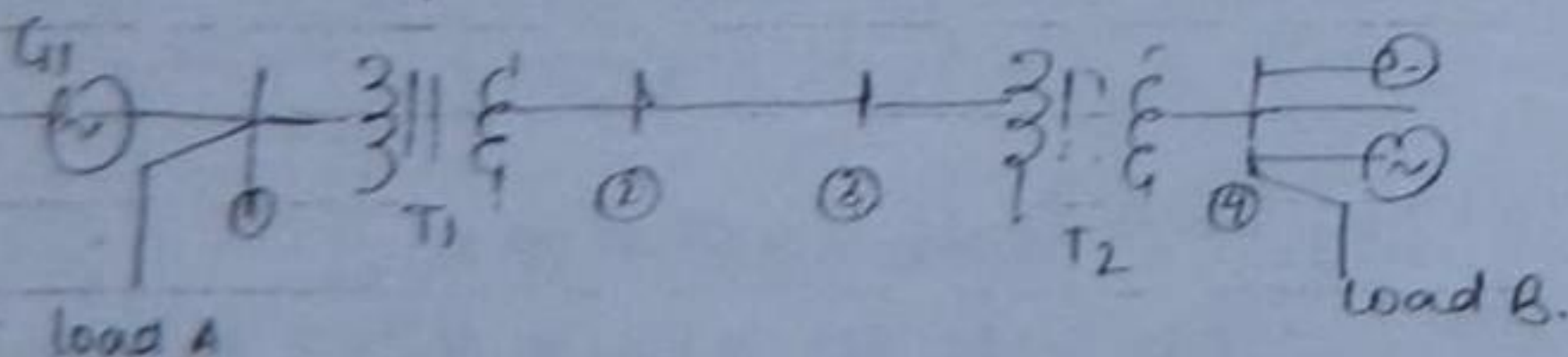b) Two loads (A) and (B) are connected to bus 1 and bus 4 respectively



Load A is 40 MW, 11 kV, 0.9 p.f lag.

represent them in reactance diagram

Solution:

$$\text{Load A} \quad V = \frac{11 \text{ kW}}{11 \text{ kV}} = 1 \text{ p.u.}$$

$$\cos \phi = 0.9 \Rightarrow \sin \phi = 0.43$$

$$P = \frac{40 \text{ MW}}{30 \text{ MVA}} = 1.33 \text{ p.u.}$$

$$P = 1.33 \text{ p.u.} \Rightarrow S = \frac{1.33}{0.9} = 1.48 \text{ p.u.}$$

$$Q = S \sin \phi = 1.48 \times 0.43 = 0.64 \text{ p.u.}$$

$$R_{\text{load A}} = \frac{V^2}{P} = \frac{1^2}{1.33} = 0.75 \text{ p.u.}$$

$$X_{\text{load}} = \frac{V^2}{Q} = 1.56 \text{ p.u.}$$

Load B

$$V = \frac{40}{60} = 1.06 \text{ p.u.}$$

$$\cos \phi = 0.5$$

$$P = \frac{40}{30} = 1.33 \text{ p.u.}$$

$$S = \frac{1.33}{0.5} = 2.66 \text{ p.u.}$$

$$Q = S \sin \phi = 2.26 \text{ p.u.}$$

represent them in reactance diagram

Solution:

$$\text{Load A} \quad V = \frac{11 \text{ kW}}{11 \text{ kV}} = 1 \text{ p.u.}$$

$$\cos \phi = 0.9 \Rightarrow \sin \phi = 0.43$$

$$P = \frac{40 \text{ MW}}{30 \text{ MVA}} = 1.33 \text{ p.u.}$$

$$P = 1.33 \text{ p.u.} \Rightarrow S = \frac{1.33}{0.9} = 1.48 \text{ p.u.}$$

$$Q = S \sin \phi = 1.48 \times 0.43 = 0.64 \text{ p.u.}$$

$$R_{\text{load A}} = \frac{V^2}{P} = \frac{1^2}{1.33} = 0.75 \text{ p.u.}$$

$$X_{\text{load}} = \frac{V^2}{Q} = 1.56 \text{ p.u.}$$

Load B

$$V = \frac{40}{60} = 1.06 \text{ p.u.}$$

$$\cos \phi = 0.5$$

$$P = \frac{40}{30} = 1.33 \text{ p.u.}$$


$$S = \frac{1.33}{0.5} = 2.66 \text{ p.u.}$$

$$Q = S \sin \phi = 2.26 \text{ p.u.}$$

* load in s.c \rightarrow constant impedance
 load in stability \rightarrow constant admittance.

$$k_{load A} = \frac{V^2/P}{1.33} = \frac{1.06^2}{1.33} = 0.84 \text{ p.u.}$$
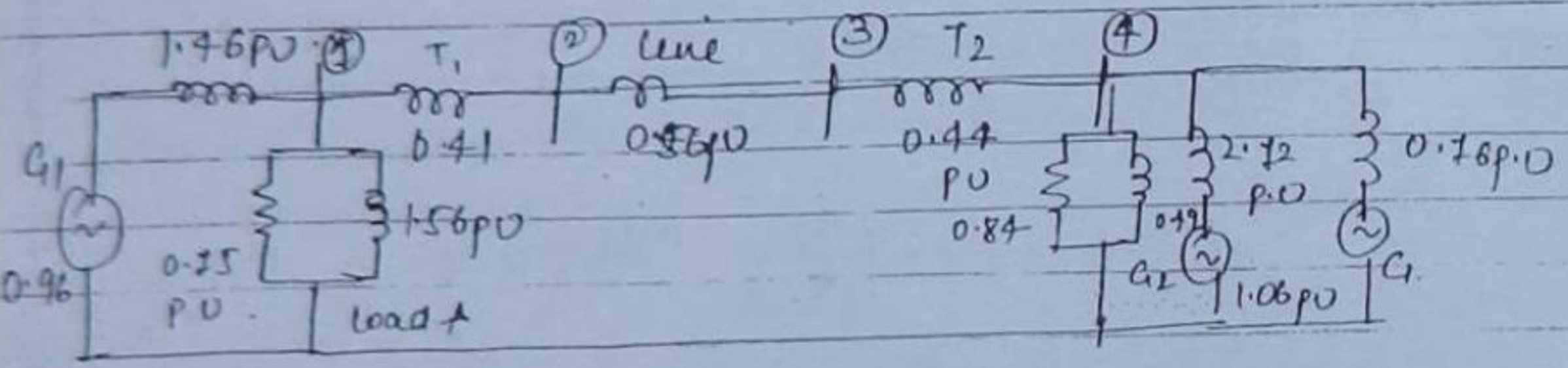
$$k_{load B} = \frac{V^2}{Q} = \frac{1.06 \text{ p.u.}}{2.28} = 0.49 \text{ p.u.}$$




$$k_{load A} = \frac{V^2/P}{1.33} = \frac{1.06^2}{1.33}$$

$$k_{load B} = \frac{V^2/Q}{2.28} = \frac{1.06 \text{ p.u.}}{2.28}$$

$$\frac{1.06^2}{1.33} = 0.84 \text{ p.u.}$$

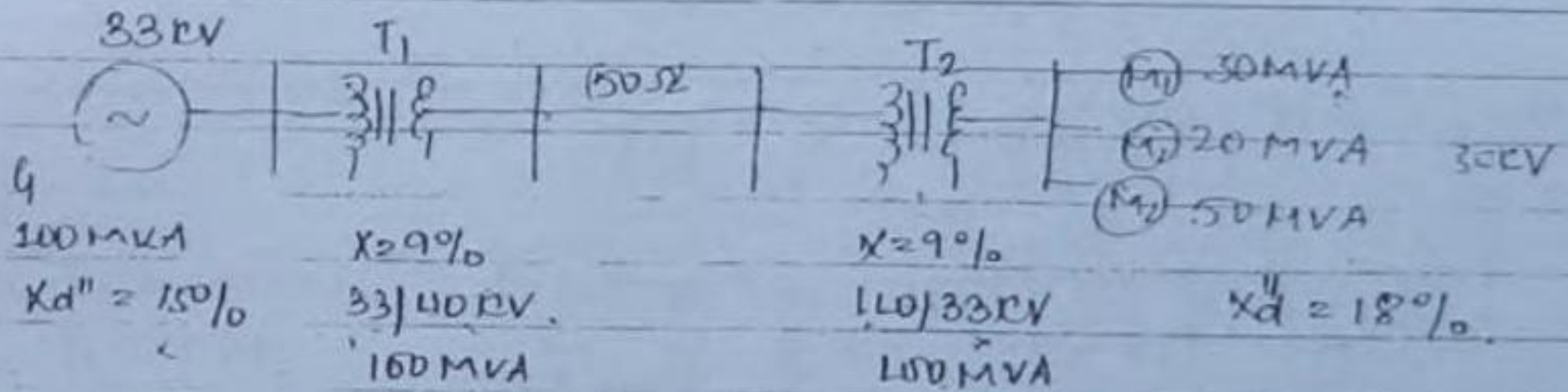Example:-

A 100 MVA, 33kV 3- ϕ gtr has sub-transient react of 15% the gtr is connected to the mtr name rate T/P 30MVA, 20, 50 MVA. At 30kV with 18% subtransient reactance the 3- ϕ T/Ps are rated at 100 MVA, 33/110kV with leakage reactance of 9%. The line has a reactance of 50 Ω obtain pu equivalent mac. diagram.



1) Common base MVA : 100 MVA

Base voltage of LV side of $T_1/T_2 = 33kV$

" " of HV side of T_1 & $T_2 = 110kV$

1) $X_{G1} = 0.15 pu$ (related value of equipment & selected base value are same)

2) $X_{T1} = 0.09 pu$ (" " ")

3) $Z_b = \frac{(kV_b)^2}{MVA_b} = \frac{(110)^2}{100} = 121 \Omega$

$$Z_b = 121 \Omega$$

$$X_{line} (pu) = \frac{50}{121} = 0.41 pu$$

$$X_{line} (pu) = 0.41 pu$$


$$4) \quad X_{T2} = 0.09 \text{ pu}$$

$$X_{m1} = X_m \left(\frac{\text{MVA}_{\text{old}}}{\text{MVA}_{\text{new}}} \right) \left(\frac{\text{KV}_{\text{base old}}}{\text{KV}_{\text{base new}}} \right)^2$$


$$= 0.18 \left(\frac{100}{50} \right) \left(\frac{30}{33} \right)^2 = 0.496 \text{ pu}$$

$$X_{m2} = 0.18 \left(\frac{100}{20} \right) \left(\frac{30}{33} \right)^2 = 0.74 \text{ pu}$$
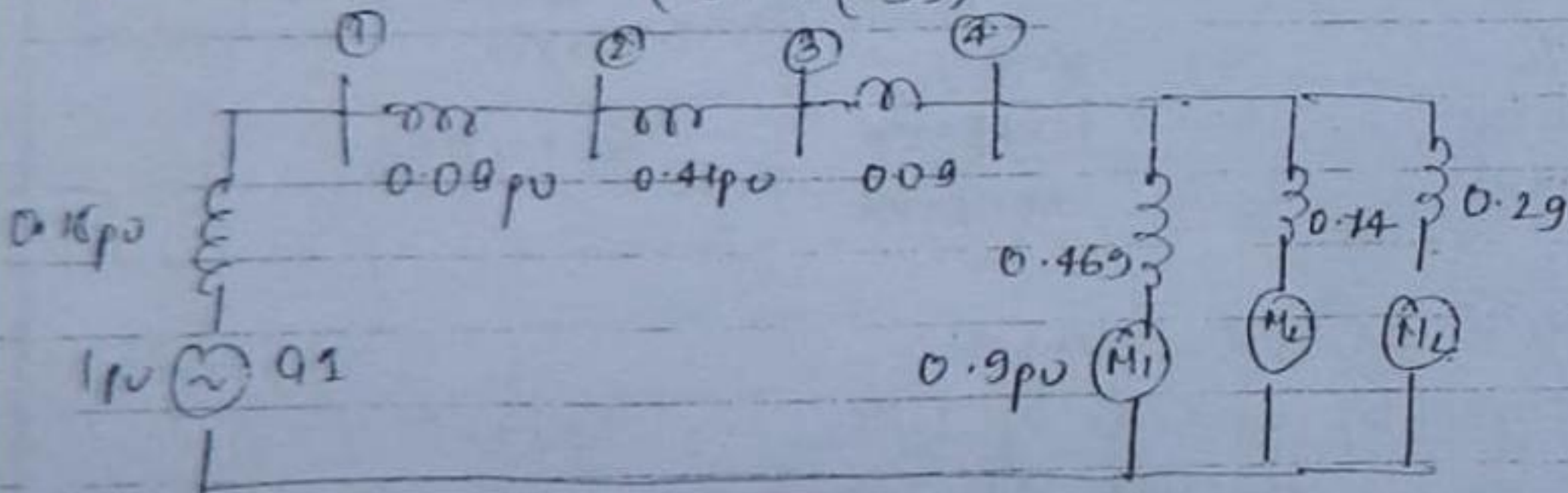
$$X_{m3} = 0.18 \left(\frac{100}{50} \right) \left(\frac{30}{33} \right)^2 = 0.24 \text{ pu}$$



Short circuit KVA:-

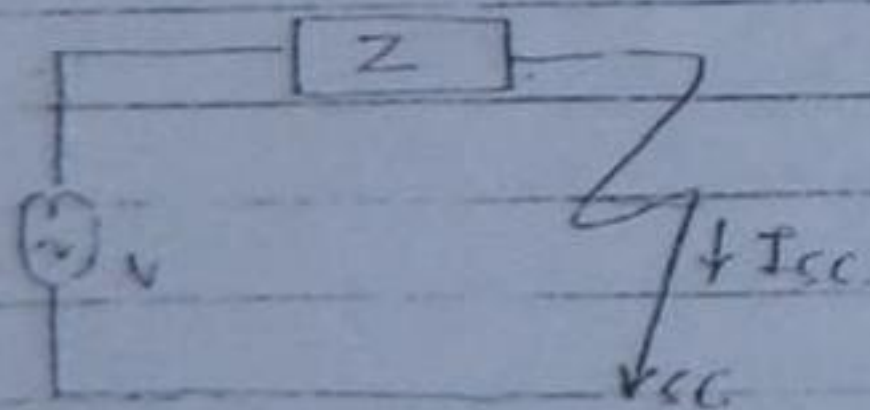

$V =$ Rated voltage

$I =$ Rated current

$Z =$ internal impedance

$$\boxed{I_{sc} = \frac{V}{Z}} \quad \text{--- (1)}$$

$$Z_{\text{base}} = \frac{V}{I}$$

$$Z_{\text{pu}} = \frac{Z}{Z_{\text{base}}} = \frac{Z}{\frac{V}{I}}$$

Note: Ratio of rated current to short ckt current of equipment given p.u impedance.

$$Z_{p0} = \frac{I}{V/2} = \frac{I}{I_{sc}}$$

$$\% Z = \frac{I}{I_{sc}} \times 100$$

$$I_{sc} = \frac{I \times 100}{\% Z}$$

$$V I_{sc} = \frac{VI \times 100}{\% Z}$$

$$\text{Short ckt KVA} = \frac{\text{Rated or base KVA} \times 100}{\% Z}$$


Procedure of short circuit calculation?

- 1) Convert the given single line diagram of power s/m. N/w into p.v equivalent impedance diagram.
- 2) Identify the fault terminal. Across the fault terminals reduce the n/w into thevenin equivalent ckt.
- 3) Using the %age thevenin equivalent impedance short ckt KVA can be calculated using the following formulae.

$$\text{Short ckt KVA} = \frac{\text{Common base KVA} \times 100}{Z_{th} \%}$$

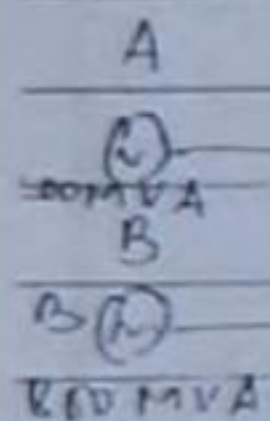Example:-

A, 2 generating station having S.C capacities of 1200 MVA, 800 MVA resp. & operating at 11 kV or linked by an interconnected cable having a reactance of 0.5Ω / phase. Determine short ckt capacities of each station. (how much power flows when SC occurs)



Cable
 0.5Ω /
phase.

Let the rated base MVA = 1200

\therefore for station A, the %X is

$$1200 = 1200 \times \frac{100}{\%X}$$

%X

$$\Rightarrow \%X_A = 100$$

Station B %age reactance is

$$800 = 1200 \times \frac{100}{\%X_B}$$

%X_B

$$\%X_B = 150\%$$


$$Z_{base} = \frac{KV_B^2}{MVA_B} = \frac{(11)^2}{1200} = 0.1008 \Omega$$

$$X_{cable} = \frac{0.5}{0.1008} = 4.96 \text{ p.u.}$$

$$\boxed{\%X_{cable} = 496\%}$$

Now we can calculate short ckt capacities of each station when fault occurs on the terminal of station (A)

and sectⁿ (B-ii').

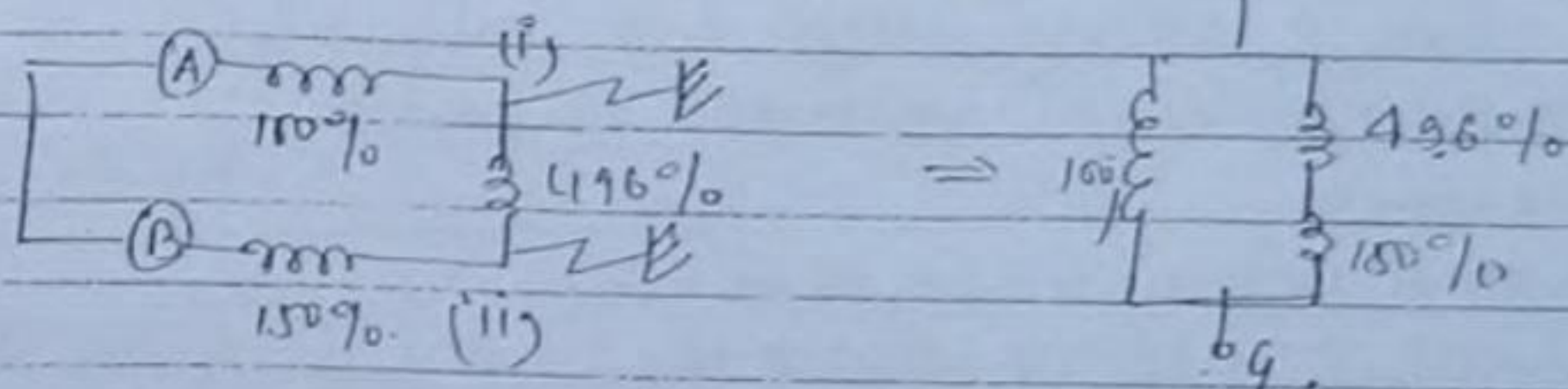


$$\%Z_{th} = 86.59\%$$

$$\text{Short circuit MVA of statⁿ A} = \frac{1200 \text{ MVA} \times 100}{86.59} = 1385 \text{ MVA}$$

When fault occurs on terminal of statⁿ B
 Short CRT MVA of stat B, $X_{th} = 119.84\%$
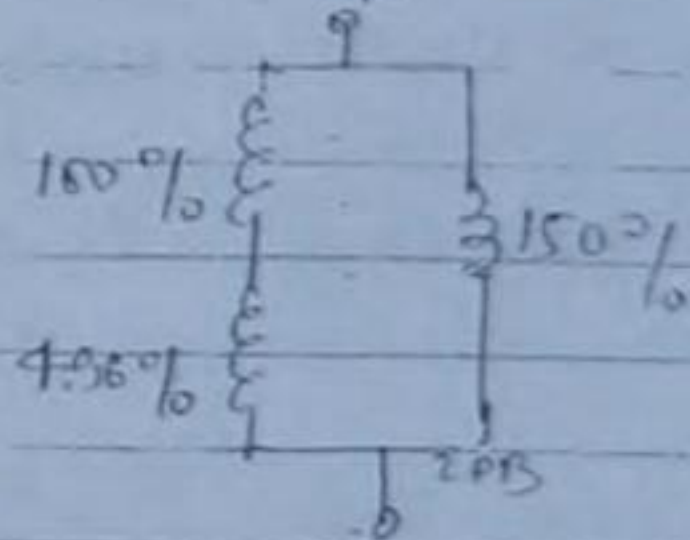
$$\text{Short circuit MVA} = \frac{1200 \times 100}{119.84} = 1001 \text{ MVA}$$



→ If we want to keep the CRT breaker at P & Q shown, then they must have breaking capacities of 1385 & 1001 MVA resp.




Quesⁿ

If we have CRT breaker of lesser capacity then how can it be effectively used?

Answer

1) To limit the short ckt current, resistance is not used due to continuous power loss.

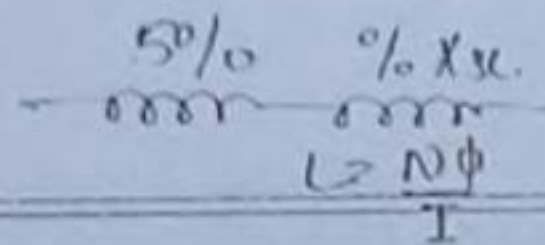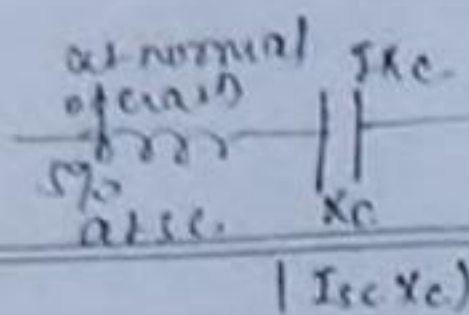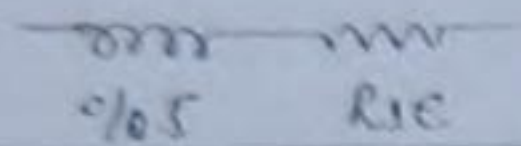2) Series capacitors are not used due to break down of dielectric during short ckt (At SC it has high voltage $I_{sc} X_c$ across & act as punctured dielectric)



3) Series Reactors are widely used but they are designed with no core material to avoid saturation problem.

(As the current starts to rise, ϕ also rises but after certain time, even increment of SC current, ϕ becomes saturated thus the value of L keeps on \downarrow ing with \uparrow ing I_{sc} & thus behaves as a short ckt path - this is becoz air core is used as ϕ in air gap is never saturated)

→ Purpose of using series reactor - to limit SC current

Purpose of using shunt reactors - to avoid ferranti effect

Series capacitors - to \uparrow steady state power limit
(As when we have inductance then power delivered is less)




shunt capacitor - → to improve P.F

* Feeder reactors are very commonly used compared to generator & bus bar reactors.

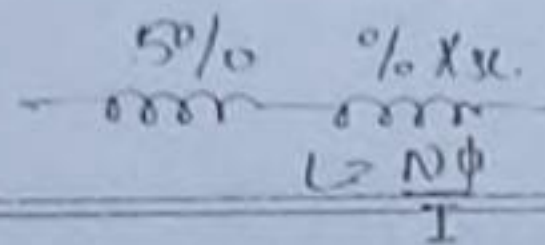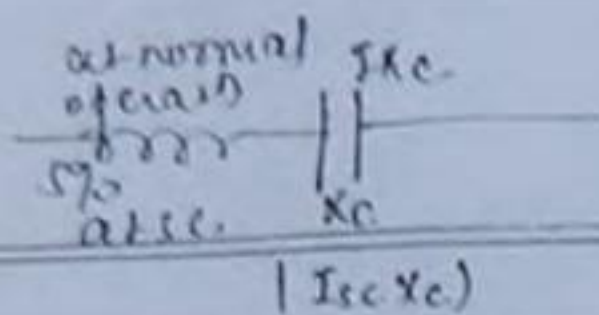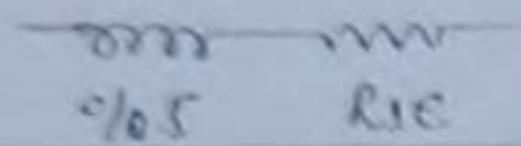Example:-

100 KVA equipment is having 5% reactance, to limit the short ckt KVA to 500 KVA the value of % Reactance used for series reactors is -

$$500 \times 2 = 100 \times \frac{100}{X_{sc}} \\ \therefore X_{sc} = 4\%$$



3) Series Reactors are widely used but they are designed with no core material to avoid saturation problem.

(As the current starts to rise, ϕ also rises but after certain time, even increment of SC current, ϕ becomes saturated thus the value of L keeps on decreasing with rising I_{sc} & thus behaves as a short ckt path - this is becoz air core is used as ϕ in air gap is never saturated)

→ Purpose of using series reactor - to limit SC current

Purpose of using shunt reactors - to avoid ferranti effect

Series capacitors - to ↑ steady state power limit
(As when we have inductance then power delivered is less)

shunt capacitor - → to improve P.F

* Feeder reactors are very commonly used compared to generator & bus bar reactors.

Example:-

100 KVA equipment is having 5% reactance, to limit the short ckt KVA to 500 KVA the value of % Reactance used for series reactors is -


$$500 \times 2 = 100 \times \frac{100}{X_{sc}} \\ \Rightarrow X_{sc} = 4\%$$

$$5\% + X_{sc} = 20$$

$$\%X_{sc} = 15\%$$

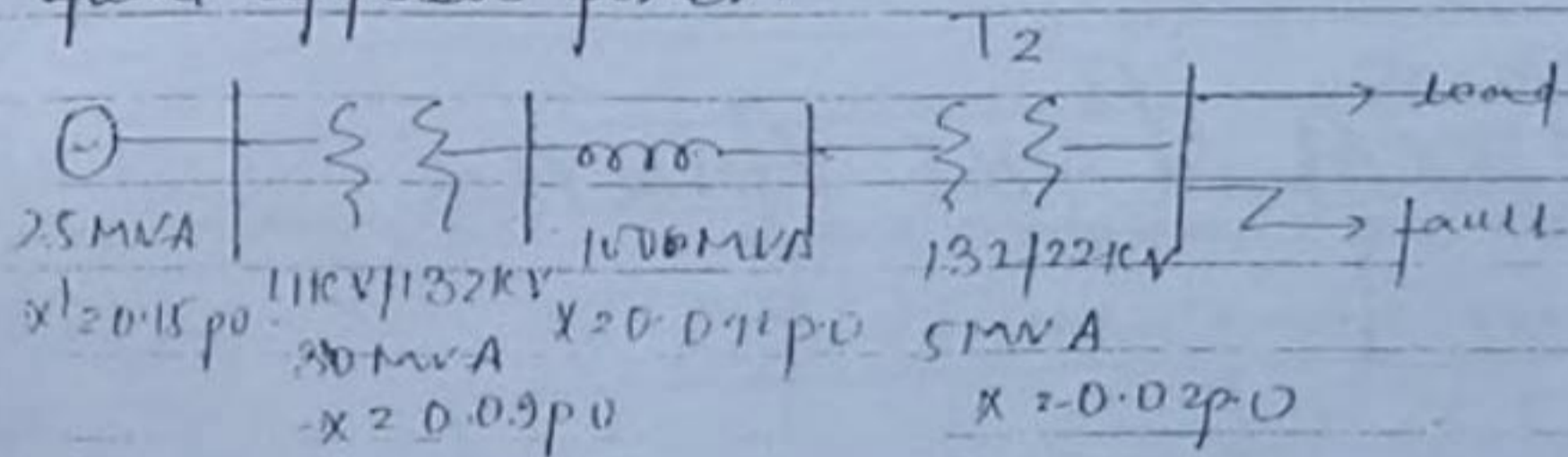Example:-

A symmetrical 3 ϕ short ckt occur on the 22kV busbar as shown in the fig. Calculate fault current and fault apparent power.



Let the common base MVA = 100 MVA

$$X_{G1} = 0.15 \times \left(\frac{100}{2.5}\right) \left(\frac{11}{11}\right)^2 = 0.6 \text{ pu}$$


$$X_{T1} = (0.09) \times \left(\frac{100}{30}\right) = 0.3 \text{ pu}$$

$$X_{line} = 0.092 \text{ pu}$$

$$X_{T2} = 0.02 \times \frac{100}{5} = 0.4 \text{ pu}$$

Base current on LV side of T2 is
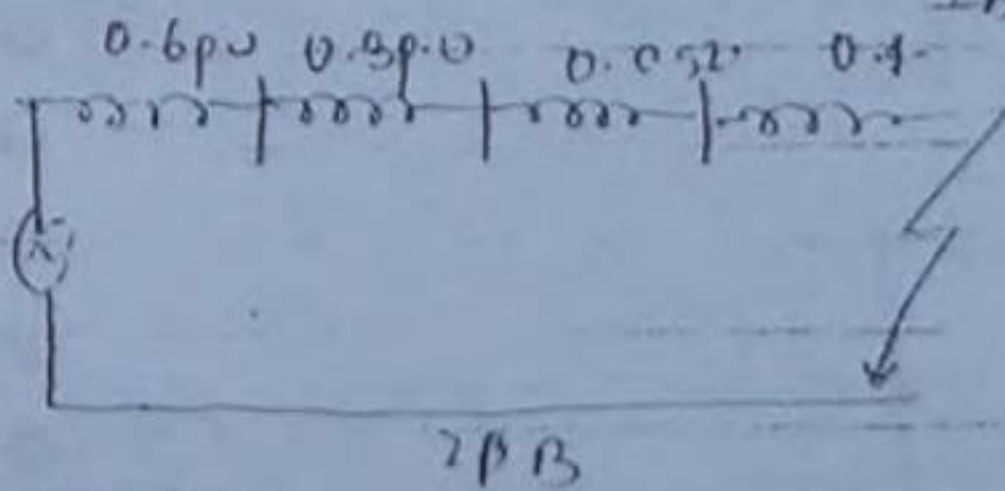
$$I_{base} = \frac{100 \times 10^6}{\sqrt{3} \times 22 \times 10^3} = 2624.31 \text{ Amp}$$



$$I_f = 1 \angle 0^\circ$$

$$= V_{10}$$


$$j(0.6 + 0.3 + 0.092 + 0.4) \text{ pu}$$

$$I_f(\text{actual}) = I_f(\text{p.u.}) \times I_f(\text{base})$$

$$I_f(\text{actual}) = 0.718 \times 26424.3 = 1884.24 \text{ Amp}$$

$$\begin{aligned} \text{Fault MVA} &= 0.718 \text{ pu} \\ &= 0.718 \times 160 \text{ MVA} \\ &= 114.88 \text{ MVA} \end{aligned}$$

UNSYMMETRICAL FAULT ANALYSIS

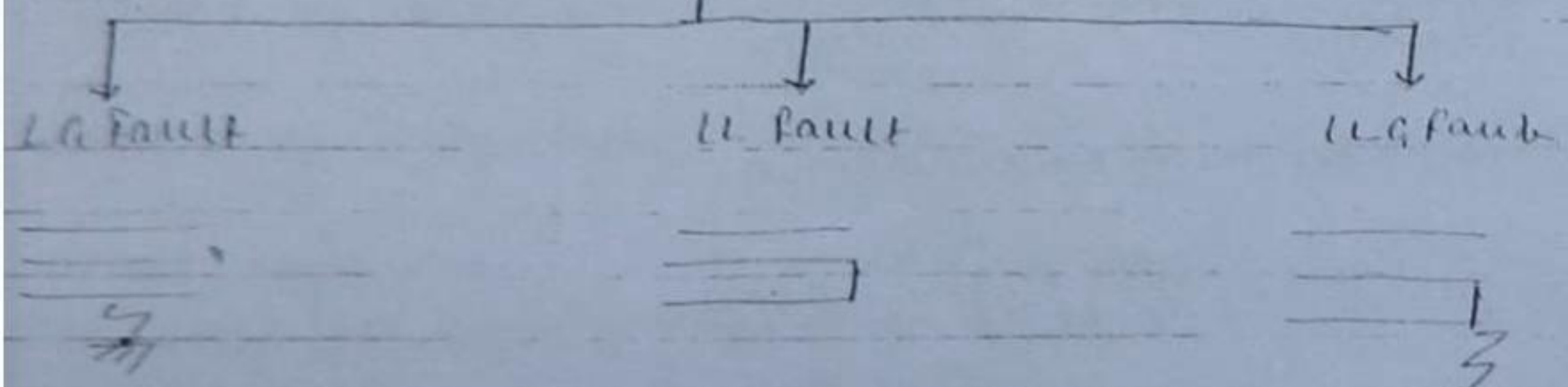


∴ Symmetrical fault all the 3φ are at different condition

∴ By working on 1-φ base, we can't claim that we have complete 3φ analysis

$$\begin{bmatrix} I_x \\ I_y \\ I_z \end{bmatrix} = \begin{bmatrix} \\ \\ \end{bmatrix} + \begin{bmatrix} \\ \\ \end{bmatrix} + \begin{bmatrix} \\ \\ \end{bmatrix}$$


$$I_R = \begin{bmatrix} I_{R1} \\ I_{R2} \\ I_{R0} \end{bmatrix} + \begin{bmatrix} I_{Y1} \\ I_{Y2} \\ I_{Y0} \end{bmatrix} + \begin{bmatrix} I_{B1} \\ I_{B2} \\ I_{B0} \end{bmatrix}$$

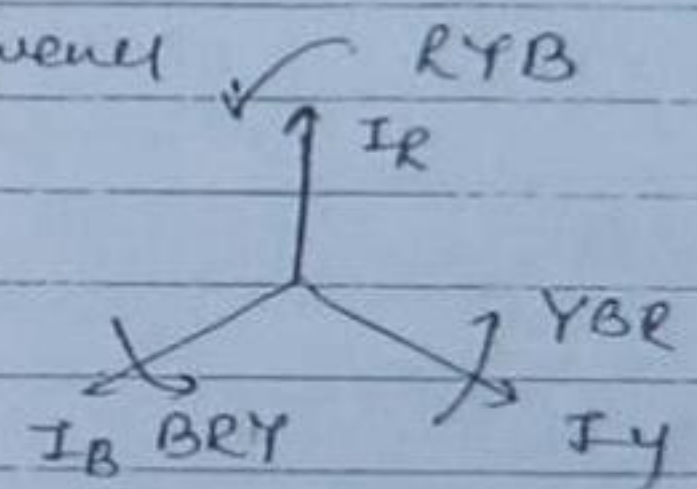\downarrow +ve sequence \downarrow -ve seq. \downarrow zero sequence




Sequence Components:

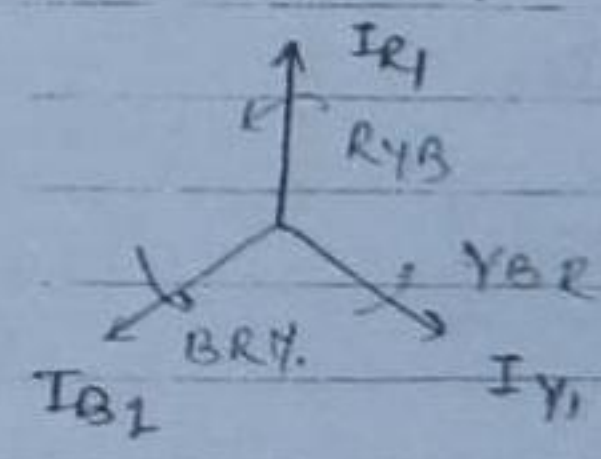+ve sequence - these component are having exactly same as the original unbalanced vectors.




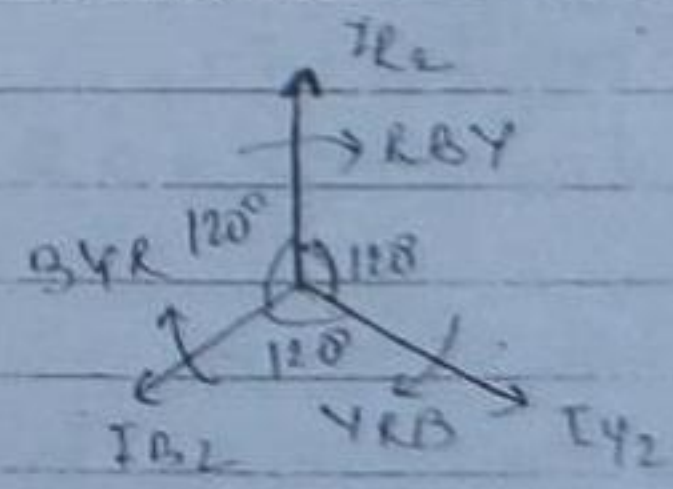-ve sequence: these component have a sequence exactly opposite to that of original unbalance vector.



Zero Sequence -

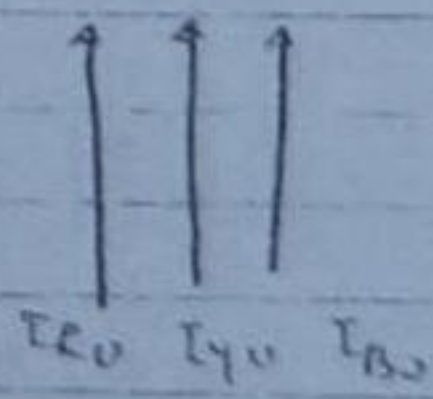these component have no sequence. (equal magnitude)




→ If we want to convert B, Y component component then we have 'd' operator

$$\begin{aligned} a &= 1 \angle 120^\circ \\ a^2 &= 1 \angle 240^\circ \end{aligned}$$

$$I_{R1} = I_{R1} \angle 0^\circ$$

$$I_{Y1} = I_{R1} \angle 240^\circ \\ a^2 I_{R1}$$
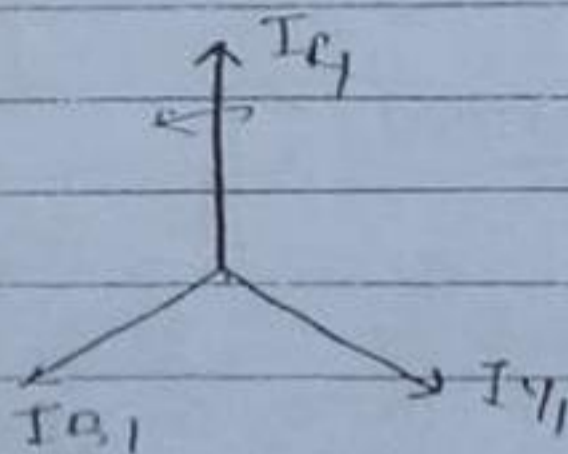
$$I_{B1} = I_{R1} \angle 120^\circ \\ a I_{R1}$$



$$I_{R0} = I_{Y0} = I_{B0}$$

$$\begin{aligned} I_{R2} &= I_{R2} \angle 0^\circ \\ I_{Y2} &= I_{R2} \angle 120^\circ \\ &= a I_{R2} \\ I_{B2} &= I_{R2} \angle 240^\circ \\ &= a^2 I_{R2} \end{aligned}$$

$$I_R = I_{R0} + I_{R1} + I_{R2}$$

$$I_Y = I_{Y0} + I_{Y1} + I_{Y2} \\ I_{R0} + a^2 I_{R1} + a I_{R2}$$

$$I_B = I_{B0} + I_{B1} + I_{B2} \\ I_{R0} + a I_{R1} + a^2 I_{R2}$$

$$\begin{bmatrix} I_{R1} \\ I_Y \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix}$$

$$\begin{aligned} [I]_{RYB} &= [A] [I]_{012} \\ [V]_{RYB} &= [A] [V]_{012} \end{aligned}$$

Relation of operator 'a' →

('a') → also known as transformation

$$\rightarrow a = 1 \angle 120^\circ = 1 (\cos 120^\circ + j \sin 120^\circ) \\ = -0.5 + j0.866$$

$$\rightarrow a^2 = 1 \angle 240^\circ = 1 (\cos 240^\circ + j \sin 240^\circ) \\ = -0.5 - j0.866$$

$$\rightarrow a^3 = 1 \angle 360^\circ = 1$$

$$\rightarrow a^4 = a^3 \cdot a = a$$

$$\rightarrow a^5 = a^3 a^2 = a^2$$

$$\rightarrow 1 + a^2 + a = 0$$

$$\rightarrow 1 - a^2 = 1 - (-0.5 - j0.866) = \frac{3}{2} + j\frac{\sqrt{3}}{2} = \sqrt{3} \left(\frac{\sqrt{3}}{2} + j\frac{1}{2} \right) \\ \sqrt{3} \angle 30^\circ$$

$$\rightarrow 1 - a = \sqrt{3} \angle -30^\circ$$


$$\rightarrow [I]_{RYB} = [A] [I]_{012}$$

$$\rightarrow [I]_{012} = [A^{-1}] [I_{RYB}]$$

$$\text{where } [A]^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a^2 \\ 1 & a & a \end{bmatrix}$$

* The original MW are mutually fixed.

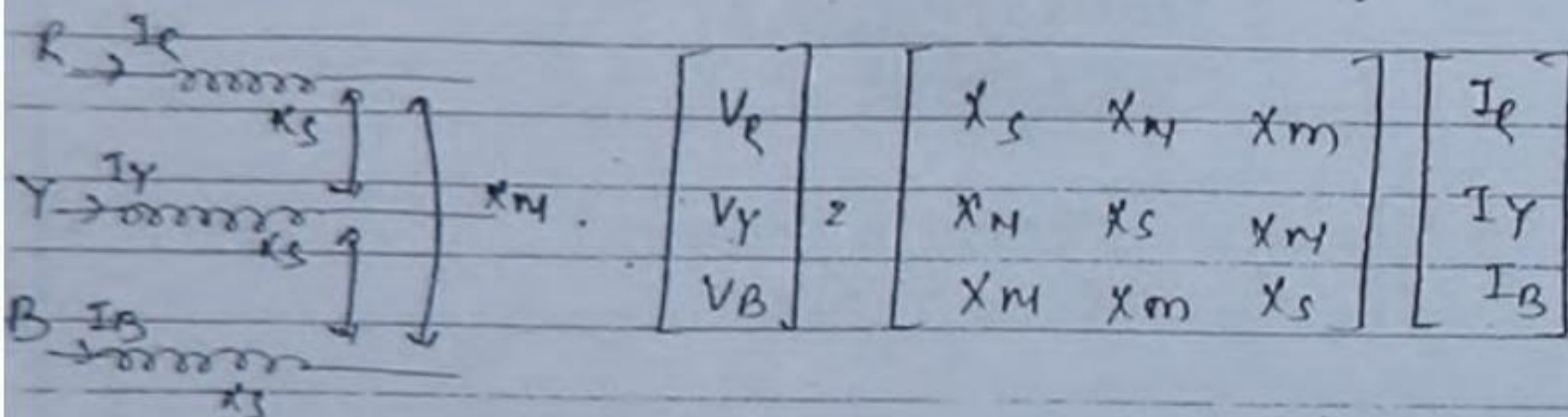* In three sequence 1ω , 2ω , 0ω , zero sequence
 N/W are mutually disjoint



$$[V]_{RYB} = [X]_{RYB} [I]_{RYB}$$

$$[A][V]_{012} = [X]_{RYB}[A][I]_{012}$$

$$[V]_{012} = [A]^{-1}[X]_{RYB}[A][I]_{012}$$

$$[X]_{012} = \begin{bmatrix} X_S + 2X_M & 0 & 0 \\ 0 & X_S - X_M & 0 \\ 0 & 0 & X_S - X_M \end{bmatrix}$$

The off diagonal elements are zero in the above matrix, we can conclude that the 1ω , 2ω , zero sequence N/W are mutually disjoint.

Example:-

A transmission line has self reactance of 50.6Ω /phase
 mutual reactance of 50.152Ω b/w any 2 phase
 find 1ω , 2ω & zero sequence reactance of the
 transmission line.

$$X_0 = X_s + 2X_m$$

$$= j0.6 + 2(j0.1)$$

$$= j0.8 \Omega$$

$$X_1 = X_s - X_m$$

$$= j0.6 - j0.1$$

$$= j0.5 \Omega$$

$$X_2 = X_s - X_m$$

$$= j0.6 - j0.1$$


$$= j0.5 \Omega$$

→ for static devices phase sequence is not imp.

Example:

On a 3 ϕ balanced s/m, the current in each phase is 10 A rms. The phase sequence is RYB. Find the sequence current. Find the sequence components.

Soln:

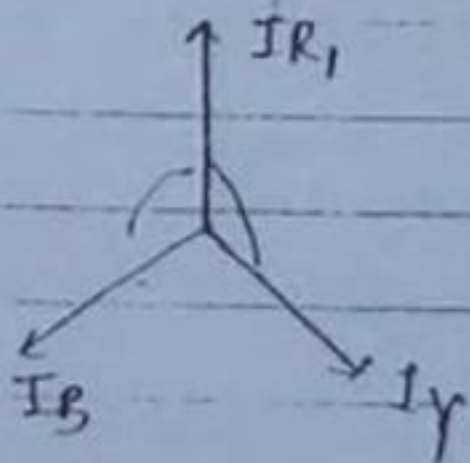

$$I_R = 10 \angle 0^\circ$$

$$I_Y = 10 \angle 240^\circ = a^2 10$$

$$I_B = 10 \angle 120^\circ = a 10$$

$$[I]_{RYB} = [A][I]_{012} = [I]_{012} = [A^{-1}][I]_{RYB}$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ a^2 10 \\ a 10 \end{bmatrix}$$

$$I_{L0} = \frac{1}{3}(L0 + a^2 L0 + a L0) = 0$$

$$I_{L1} = \frac{1}{3}(L0 + a^3 L0 + a^3 L0) = 10$$

$$I_{L2} = \frac{1}{3}(L0 + a^4 L0 + a^2 L0) = 0$$

→ By this we can say that in a balanced s/m the only current in the N/C is the sequence current.

Example:-

The fuse in Y & B are removed. Find seq component

$$10 \angle 0^\circ = I_L = 10 \angle 0^\circ$$

$$I_Y = I_B = 0$$

$$\begin{bmatrix} I_{L0} \\ I_{L1} \\ I_{L2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$I_{L1} = I_{L2} = I_{L0} = 10/3 \text{ A}$$

SEQUENCE IMPEDANCES:

Generator:-

$$X_{C11} \approx X_{C12}$$

the seq reactance (-ve seq reactance)

[strictly speaking X_{C2} is slightly less than X_{C1}]

$$X_{a1} \begin{cases} \rightarrow X_{a1} = \frac{X_d'' + X_{a2}''}{2}, \frac{X_d' + X_{a2}'}{2}, \frac{X_d + X_{a2}}{2} \\ \rightarrow X_{a1} = X_d'', X_d', X_d. \end{cases}$$

(cylindrical) $\frac{r}{r}$


$$X_{G0} \ll X_{a1}$$

- for static devices like (TIF & Transmission line)

$$X_1 = X_2$$



$$X_0 \gg X_1$$

Sequence NIW:-

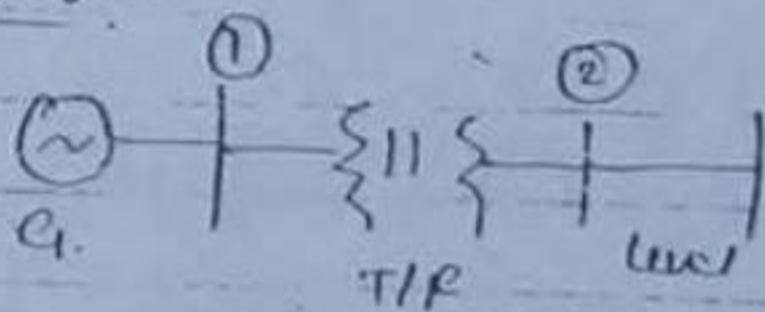


Generator Representation:-

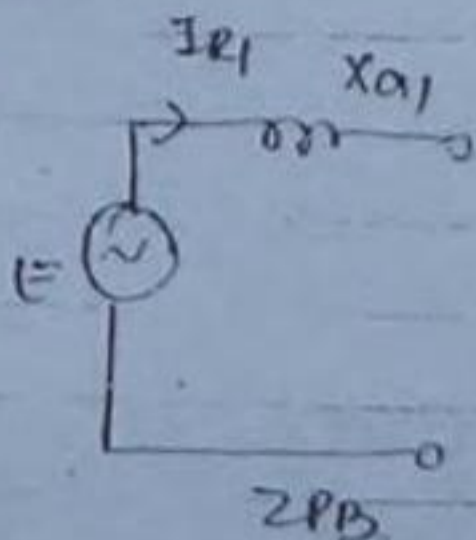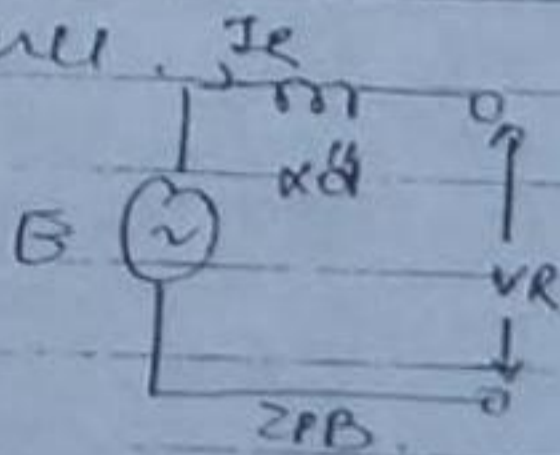
In original NIW with symmetrical fault analysis Gen. is used as const voltage element behind the reactance.




(positive)

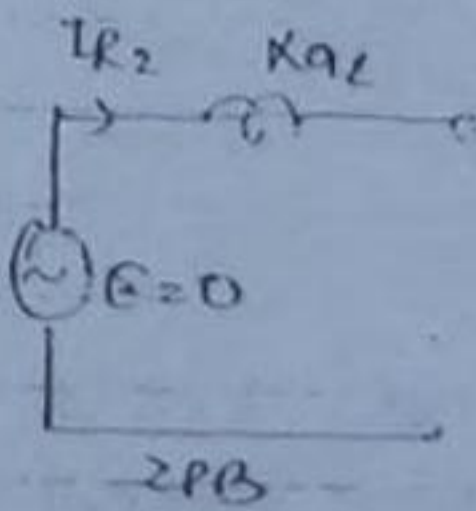

(Negative)

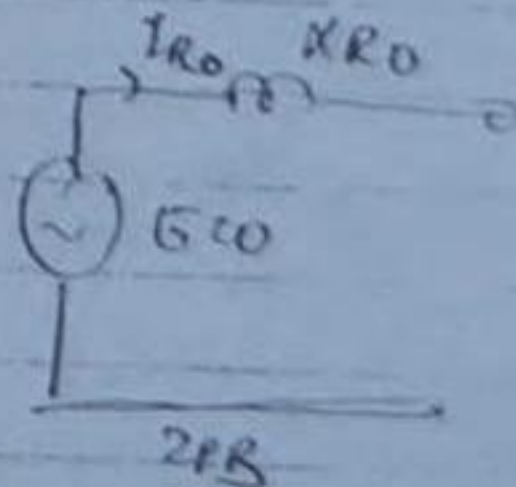

(zero)

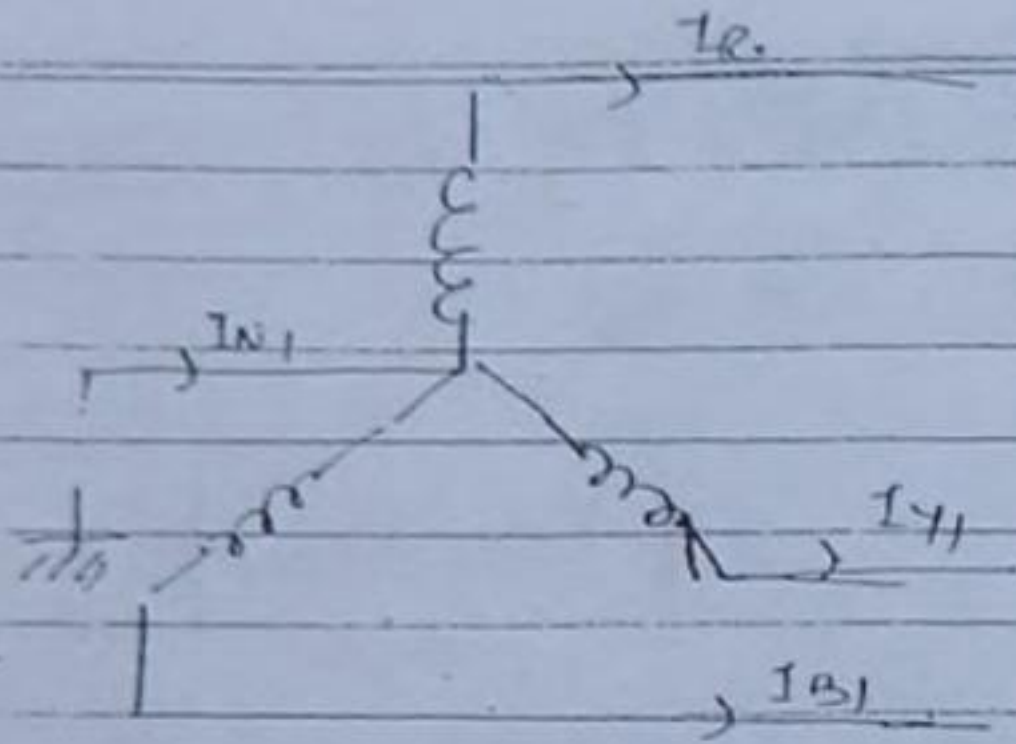

$$I_N = I_{R1} + I_{Y1} + I_{B1}$$


$$= (I_{R1} + I_{Y1} + I_{B1}) + (I_{R2} + I_{Y2} + I_{B2}) + (I_{R0} + I_{Y0} + I_{B0})$$

$I_{N0} = \text{sum of outgoing current} = 0$

$$I_N = 3I_{R0}$$



∴ positive seq current will flow whether neutral is grounded or not

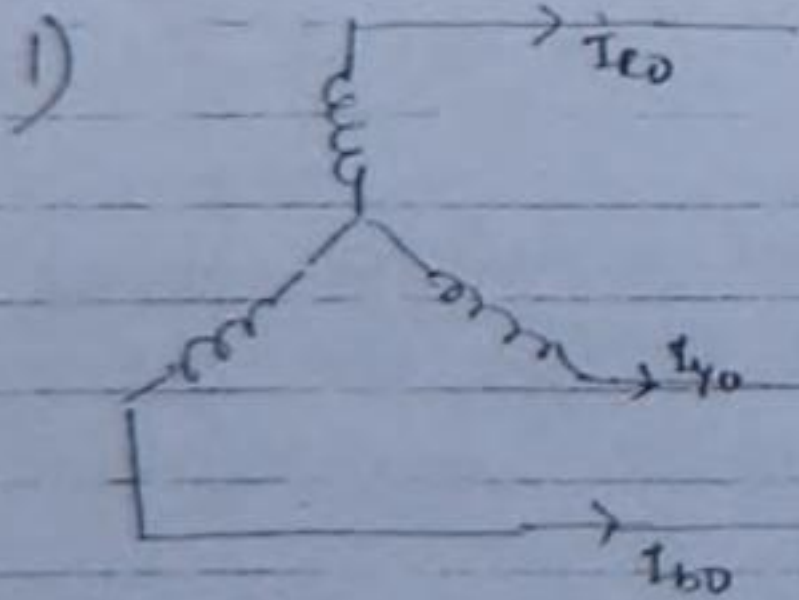→ If neutral grounded with inductor then:-





sum of incoming current = 0
 sum of outgoing current = $3I_{R0}$
 KCL not satisfied.
 So such current does not exist

∴ open circuit

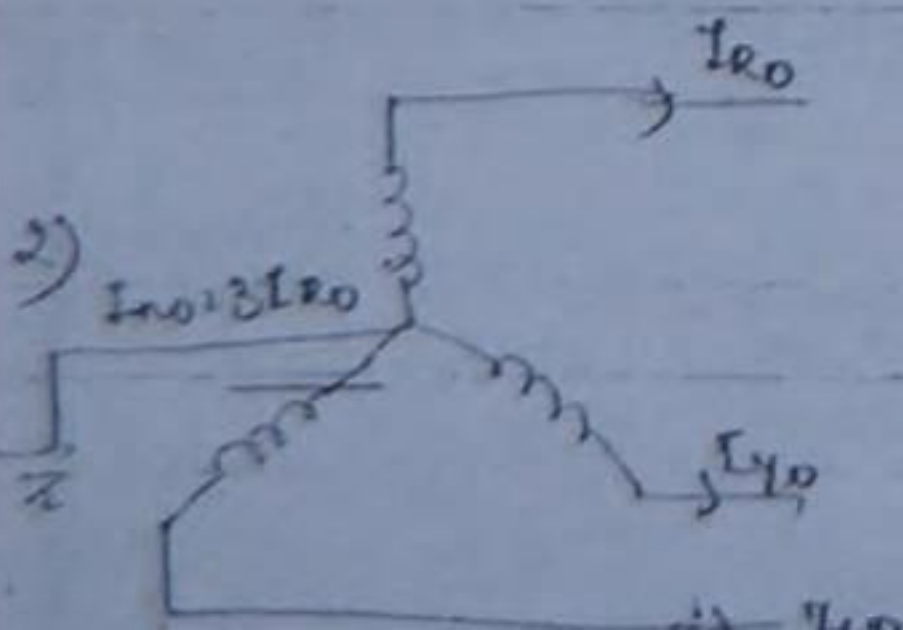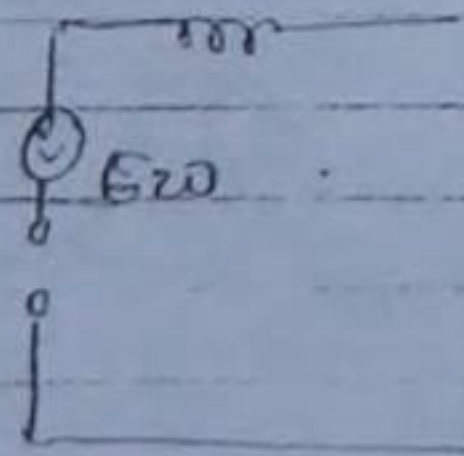

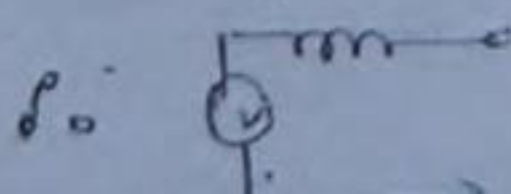Here KCL is satisfied so now current can flow



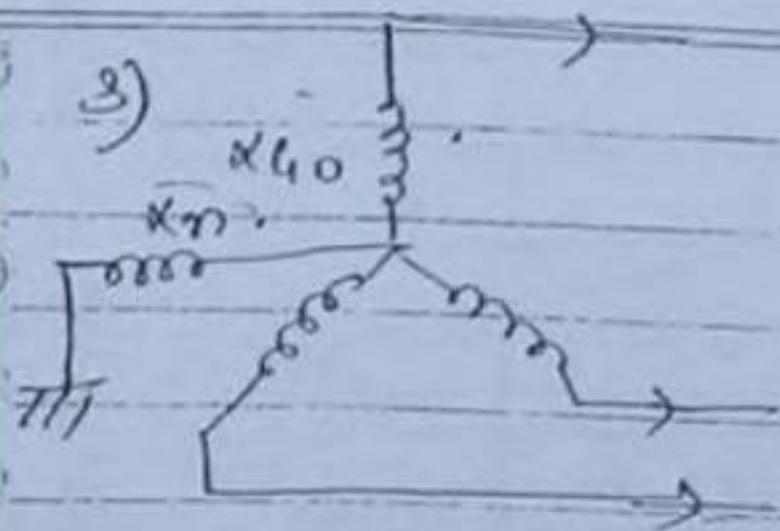

Now neutral is not ZPB
 it has drop of $3 I_{n0} X_n$.
 \therefore unbalanced condⁿ.

$$V_{R1} = 3 I_{R0} X_{R0} + I_{n0} X_{G0}$$

$$X_0 = (X_{G0} + 3X_n)$$


Notes

- 1) Only positive seq n/w contain voltage source
- 2) Negative & zero seq do not contain voltage source
- 3) Condition of neutral has got no effect in the representatⁿ of gen. both in +ve & -ve seq n/w





4) However, conditⁿ of neutral has got effect in the representatⁿ of gen, in the zero seq n/w
 If neutral is unloaded show open ct. If neutral is solidly grounded show a s.c.
 If the neutral is grounded with reactance X_n , $3X_n$ must be added to zero sequence reactance of g/w. X_{G0} to get total zero sequence reactance

$$X_0 = 6 \cdot X_{G0} + 3X_n$$

Transformer Representatⁿ

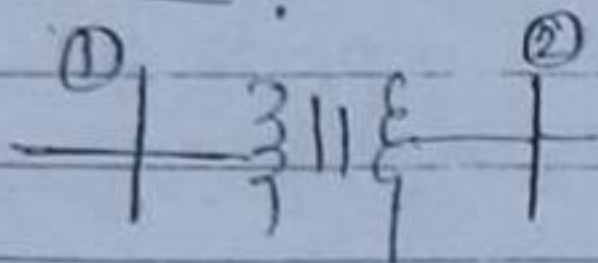

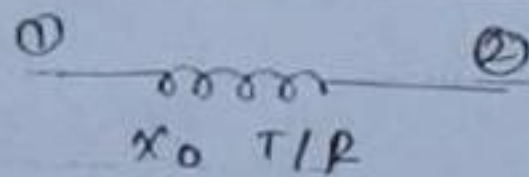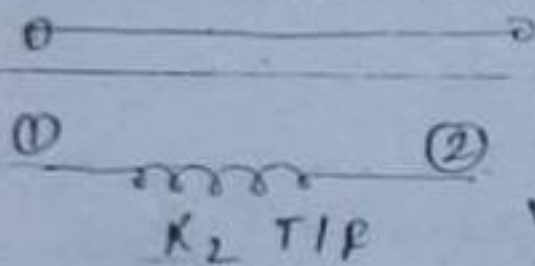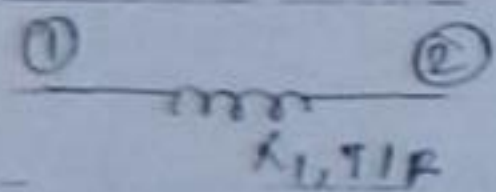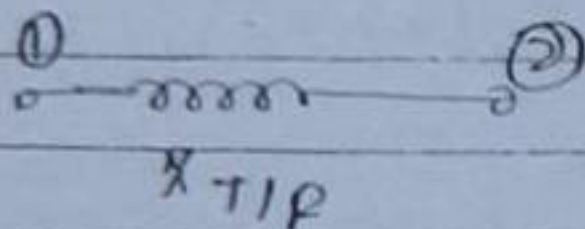→ so original n/w T/F is shown as series reactance.



ZPB

ZPB



ZPB

positive
Seq.


Negative
Seq.

Zero
Seq.

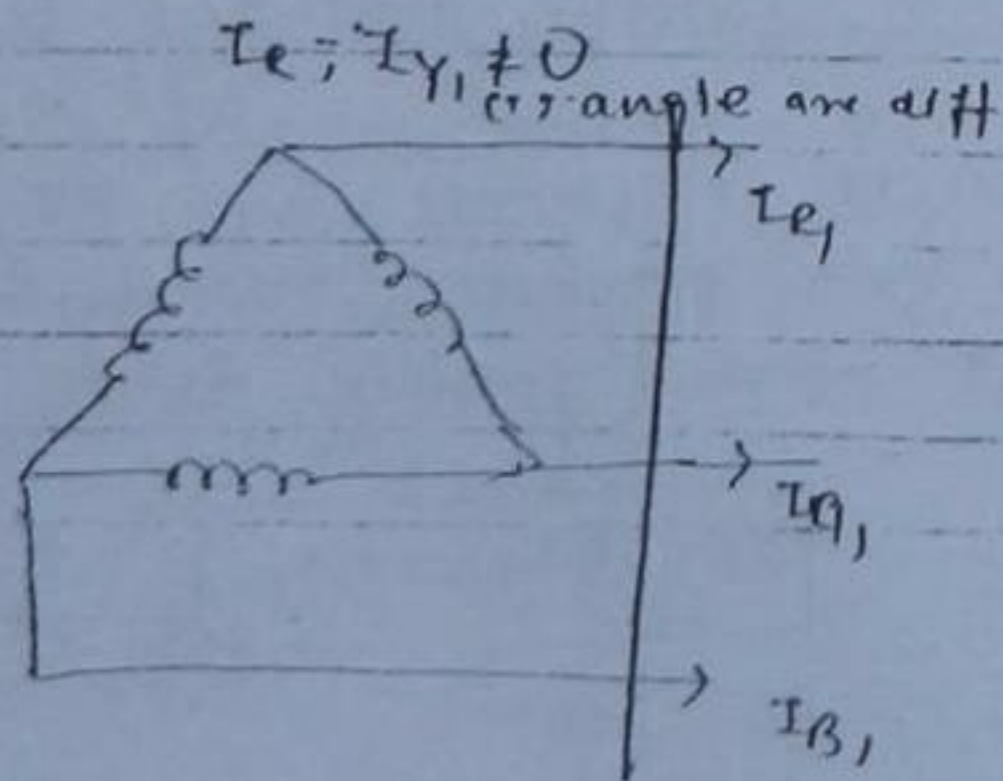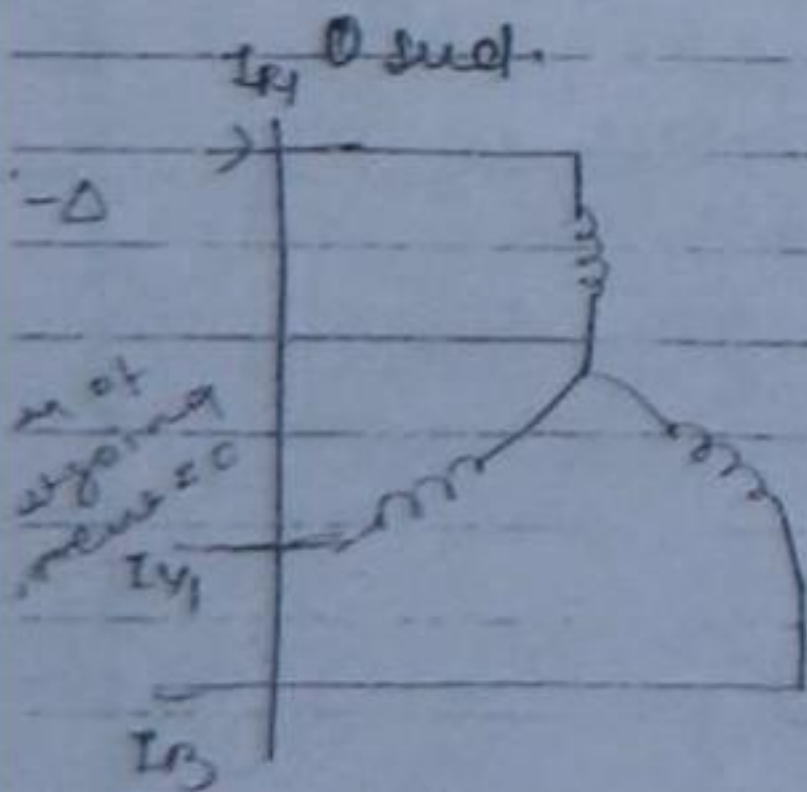→ lower X_{new} primary & secondary. can be connected in both star & delta.



∴ type of winding has no relation of T/F

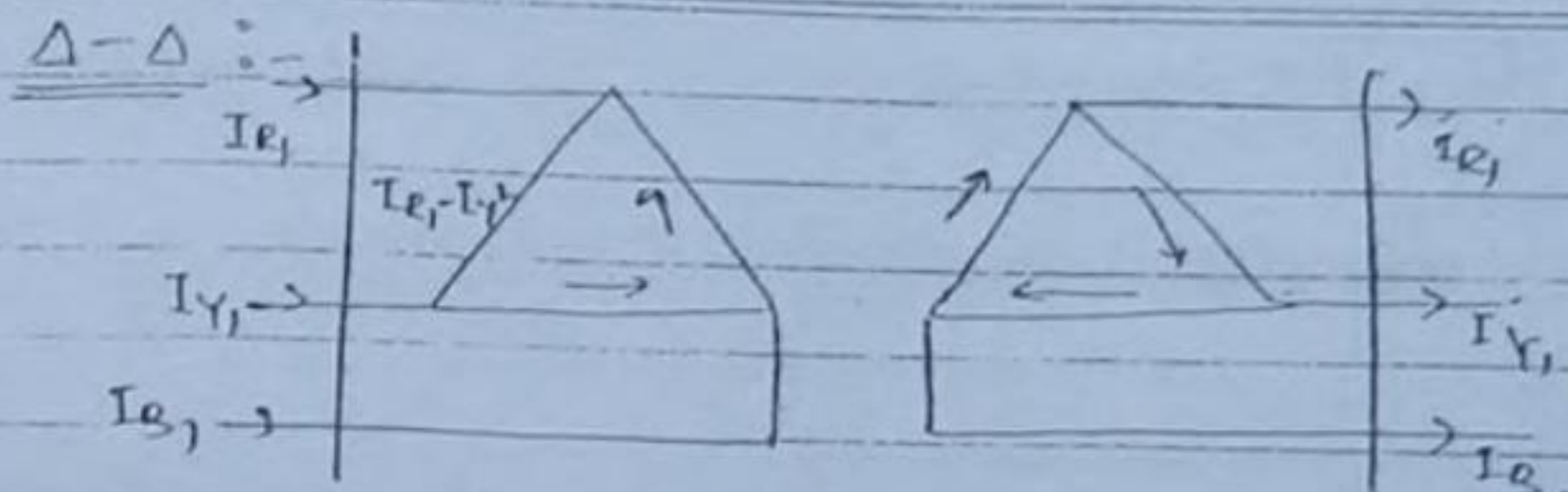

Conclusion:


x_{mes} has no effect of type of n/w whether γ or Δ no effect due to neutral ground

$I_{e1} - I_{y1} \neq 0$



\therefore mag is same but phase angle $= 120^\circ$

Zero Sequence:


1) $\gamma - \Delta$

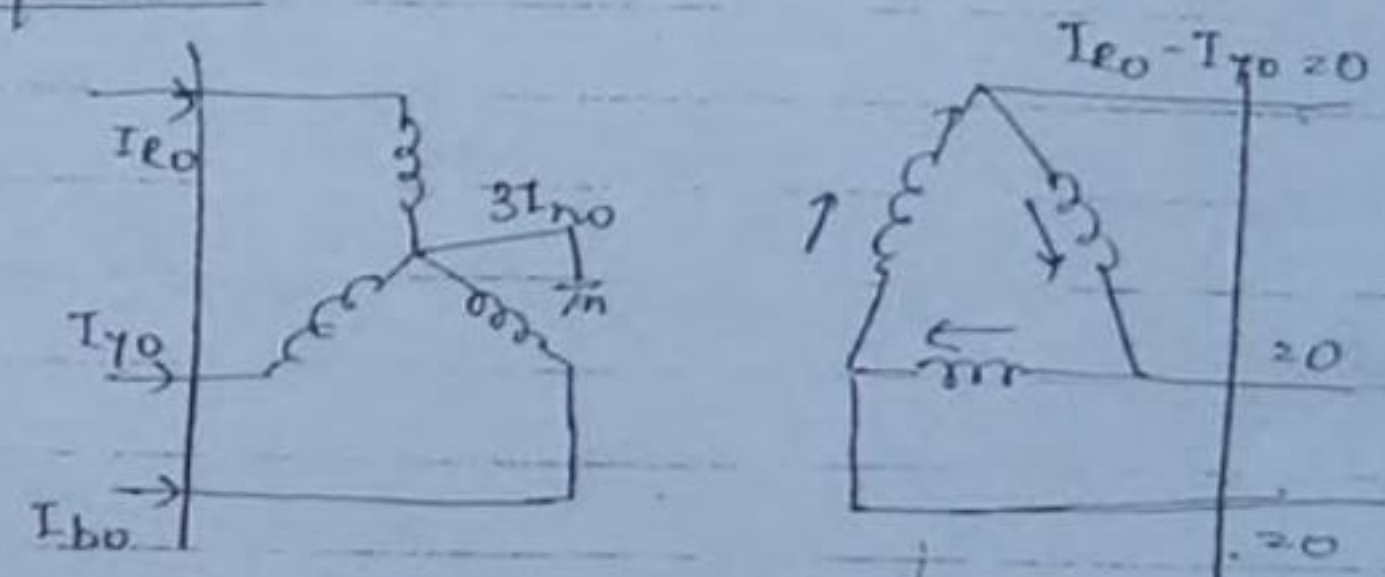

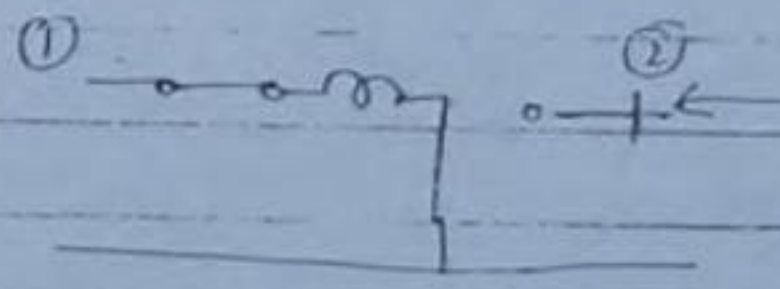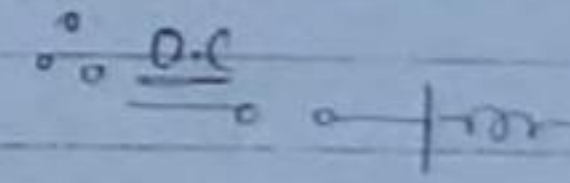
KCL is not satisfied \therefore in coming $> 3I_n$ outgoing $= 0$



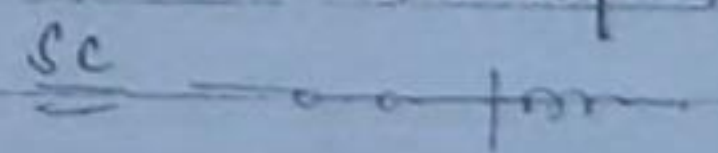\rightarrow If star point is grounded then KCL is satisfied




2) $\gamma - \gamma$

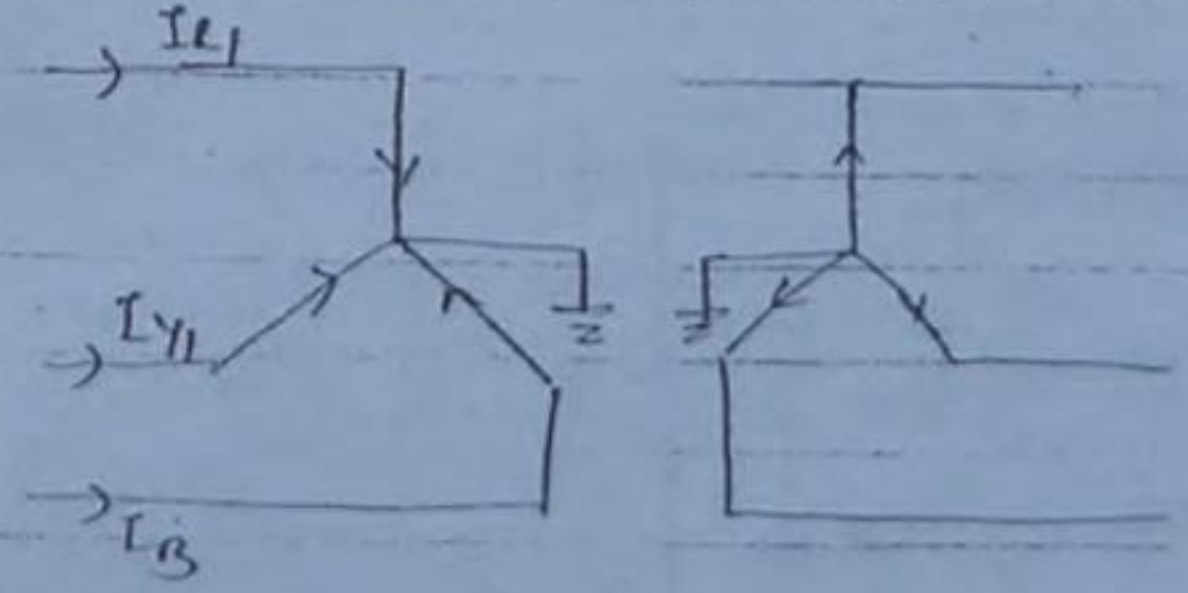


→ If secondary is ungrounded.



→ If it is grounded.

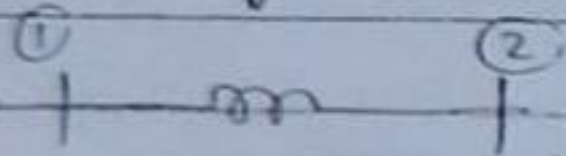

SWITCH DIAGRAM:

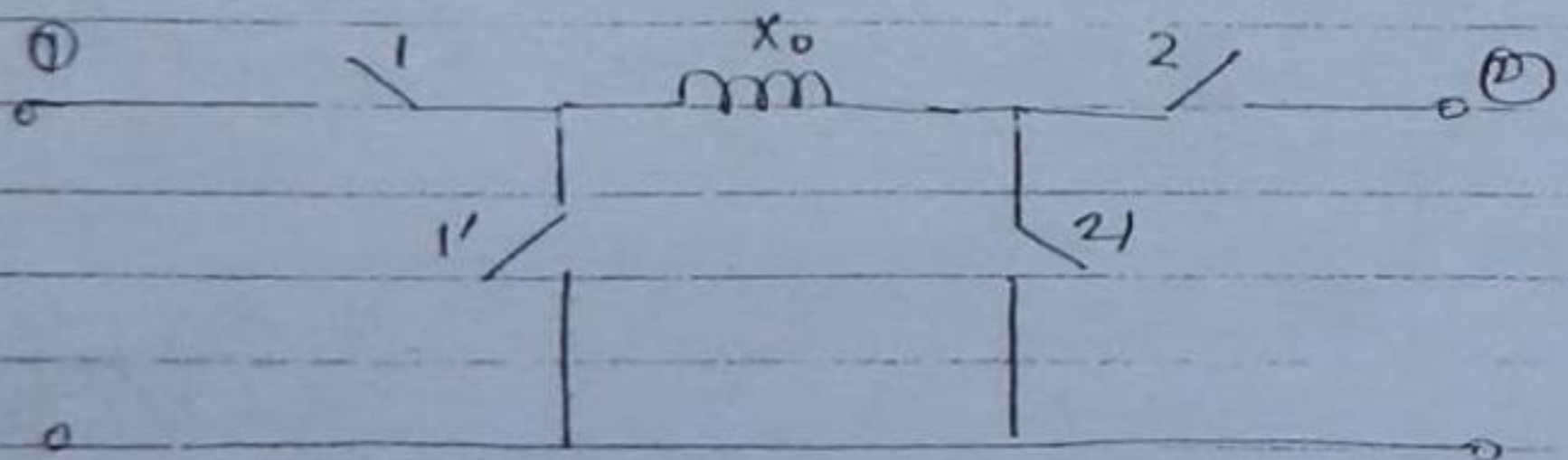


*



1, 1'	→	Primary
2, 2'	→	Secondary
1, 2	→	Series switches
1', 2'	→	Shunt switches

Representation of Transmission Line -

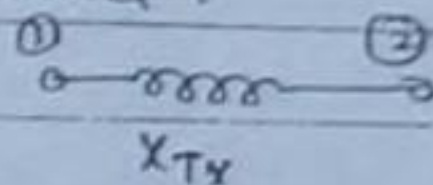On symmetrical fault represented as series reactance.





① +ve sequence

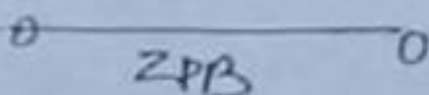
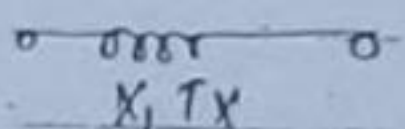


→ No conditⁿ for T.L

② -ve sequence

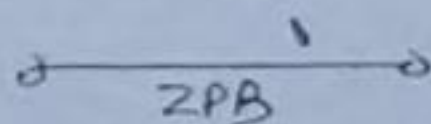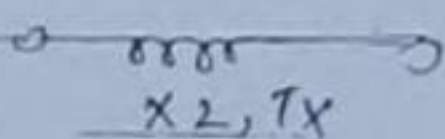


③ Zero sequence

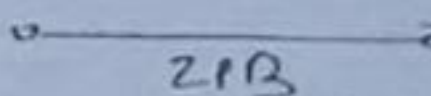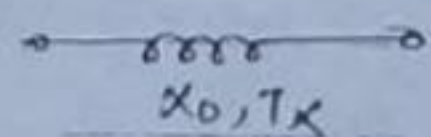

* Without verifying any conditⁿ a T.L can be simply represented as series reactance element in all 3-sequence n/w

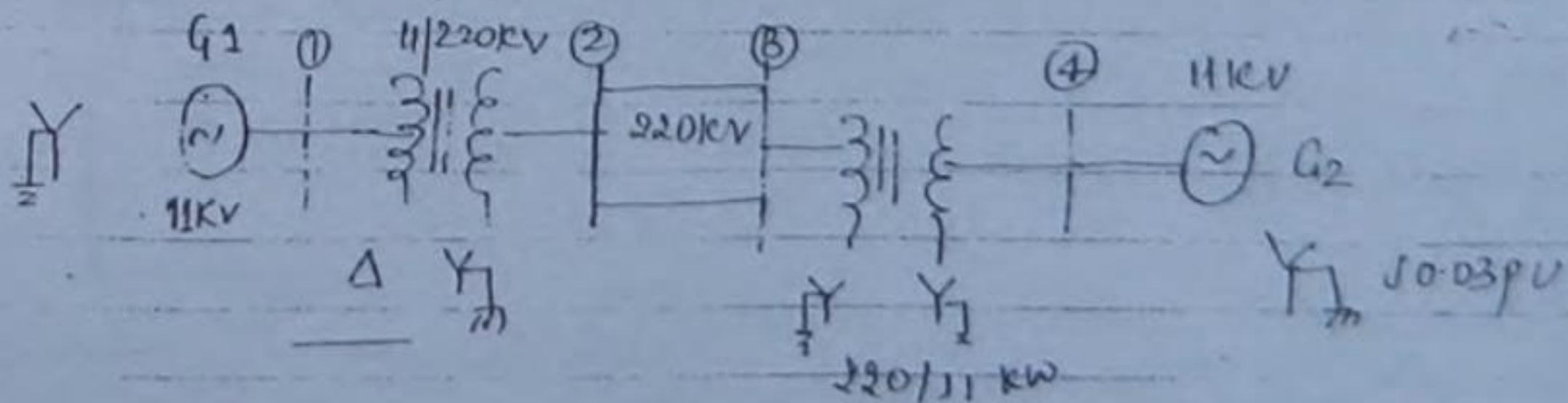Problem:-

Obtain the 3-sequence n/w for the n/w shown in figure



$\rightarrow G_1 \rightarrow X_1 = X_2 = j0.25 \quad ; \quad X_0 = j0.05 \text{ pu.}$

$G_2 \rightarrow X_1 = X_2 = j0.2 \quad ; \quad X_0 = j0.05 \text{ pu.}$


$T_1 \rightarrow X_1 = X_2 = X_0 = j0.06 \text{ pu.}$

$T_2 \rightarrow X_1 = X_2 = X_0 = j0.07 \text{ pu.}$

$L_1, L_2 \rightarrow X_1 = X_2 = X_0 = j0.3.$


Common base MVA = 100.

Solution: \downarrow

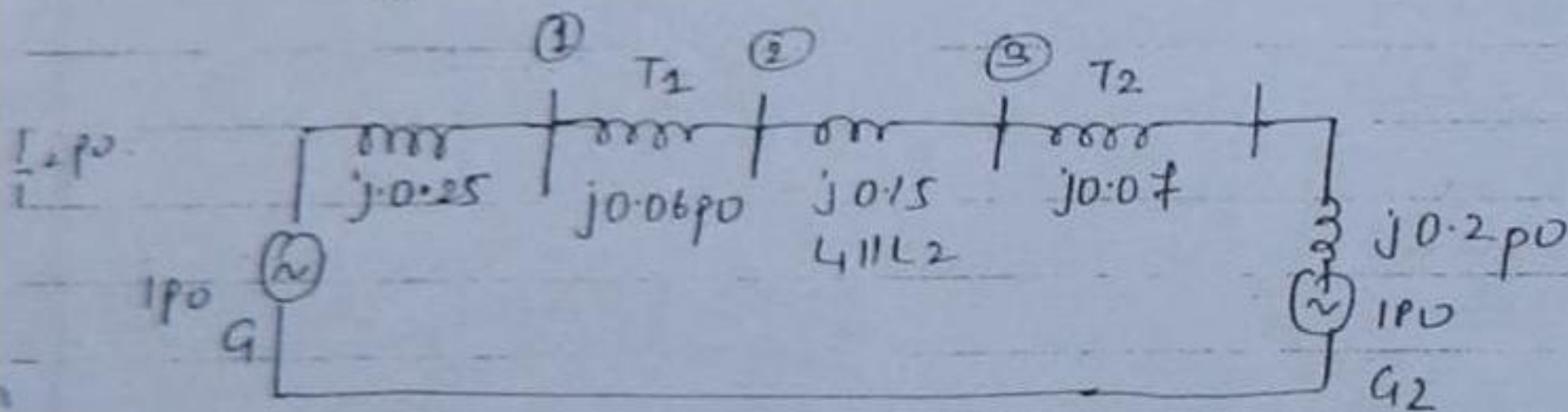


\hookrightarrow Positive sequence N/W.

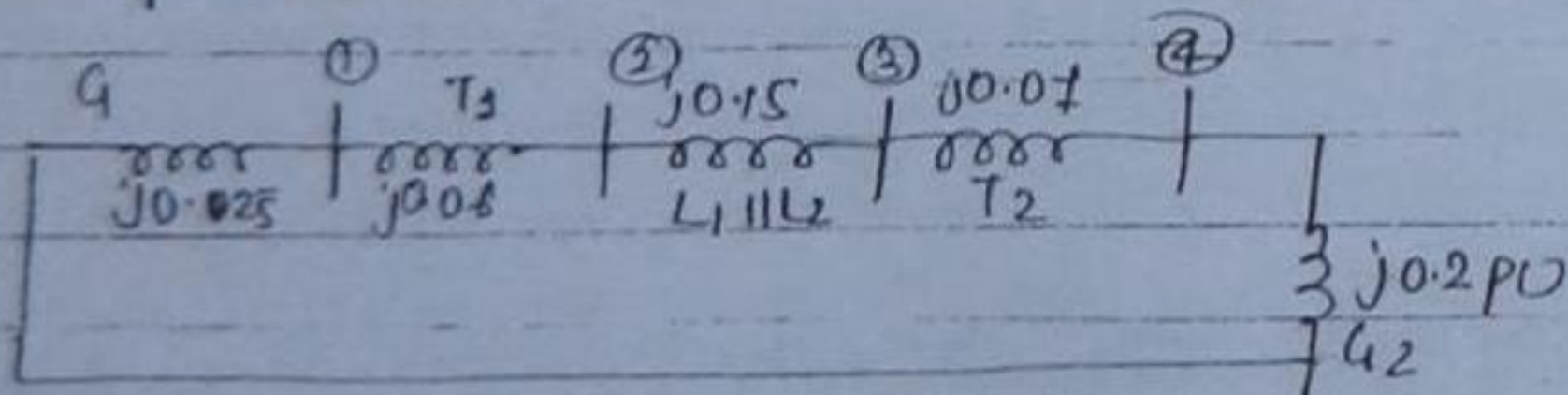Negative sequence N/W: (without voltage source rest same)



Zero sequence N/W:

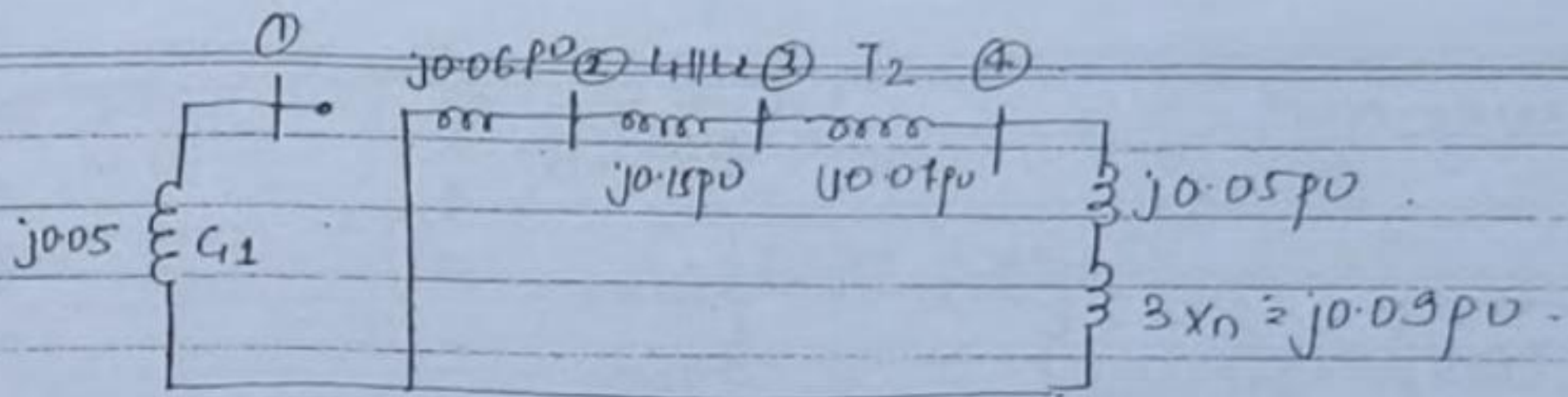

2



Part B

Let the fault is occurred on bus (3), reduce the 3-sequence n/w into thevenin equivalent n/w.


∵ in the voltage on both side is same so circulating current is zero, so drop. is also zero, so the same voltage 1 pu appears across bus (3) (parallel).

Thevenin's equivalent

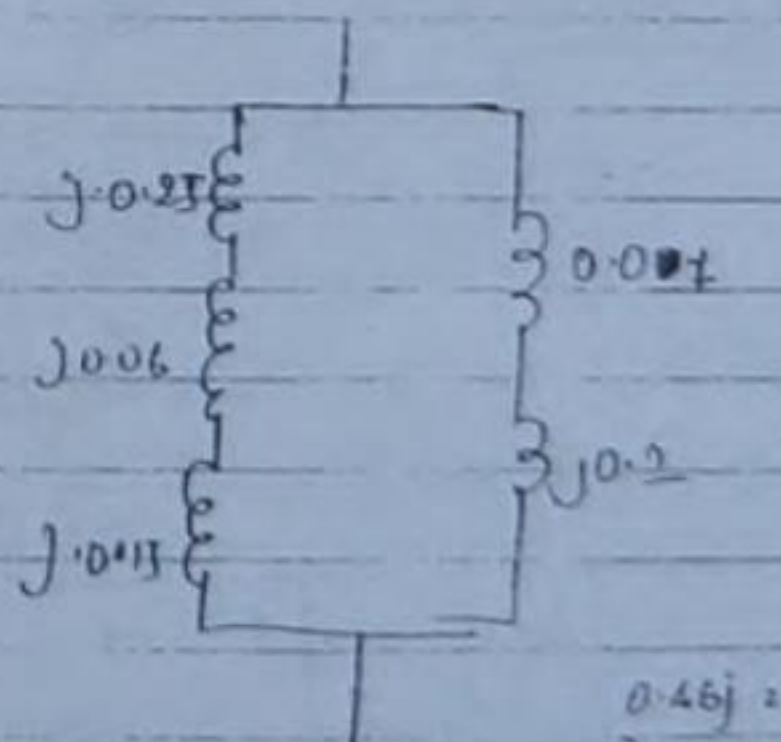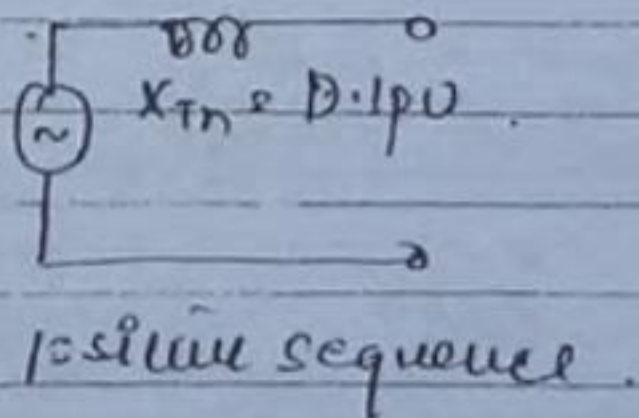$V_m = 1 \text{ pu} ; X_{Tn} = j0.17 \text{ pu}$





-ve sequence n/w same ∴ no voltage

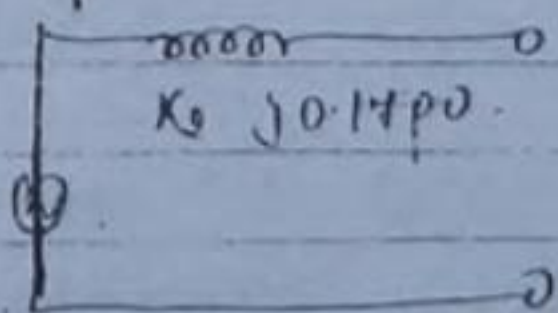

0.23 pu




Zero sequence n/w flow 4m (42)

→ Zero sequence n/w's.

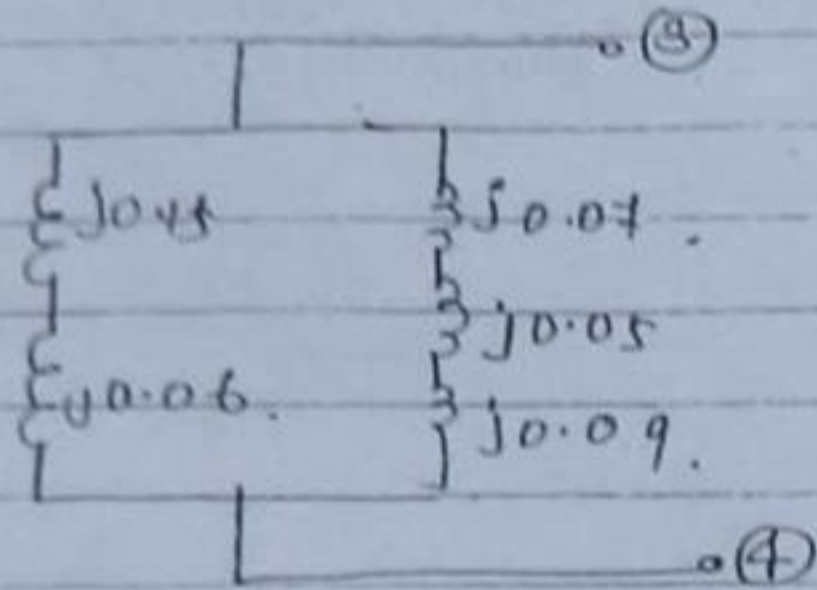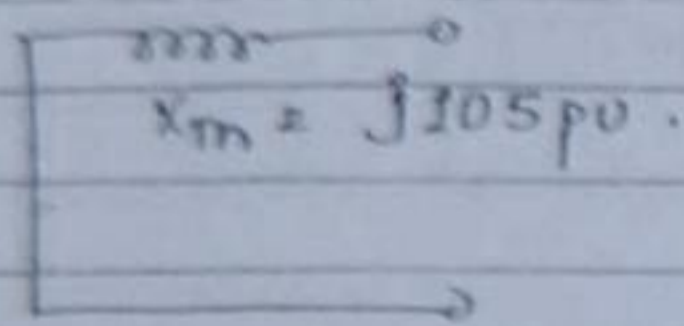

0-21C

Voltage Sequence:-

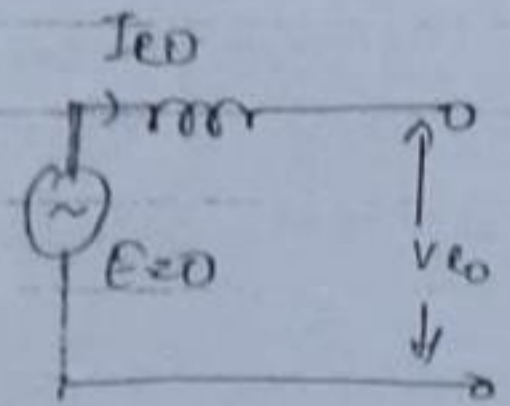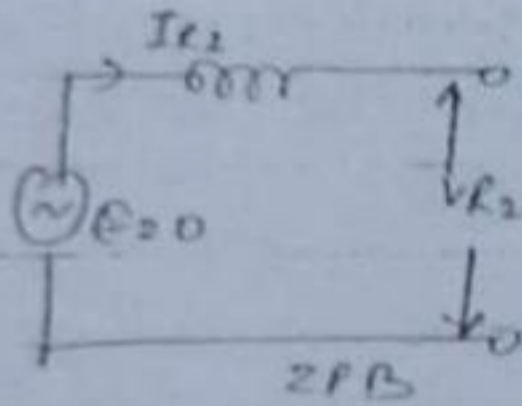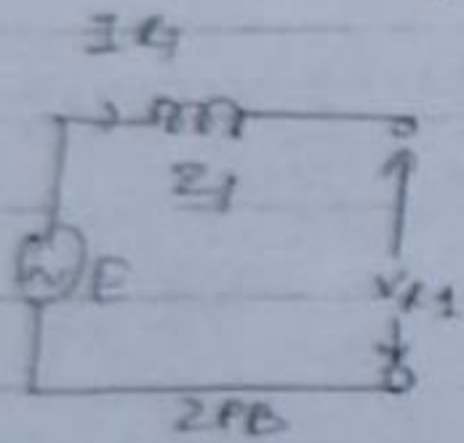

$$V_{R1} = E - I_{e1} Z_1$$

$$V_{R2} = E - I_{e2} Z_2$$

$$V_{R0} = E - I_{e0} Z_0$$

$$V_{R2} = -I_{e2} Z_2$$

$$V_{R0} = -I_{e0} Z_0$$

Positive S.


Negative

Zero

$$\begin{bmatrix} V_R \\ V_Y \\ V_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} V_{R0} \\ V_{R1} \\ V_{R2} \end{bmatrix}$$

→ Power c/w not connected to c/w is distributed c/w

Single line Ground Fault:

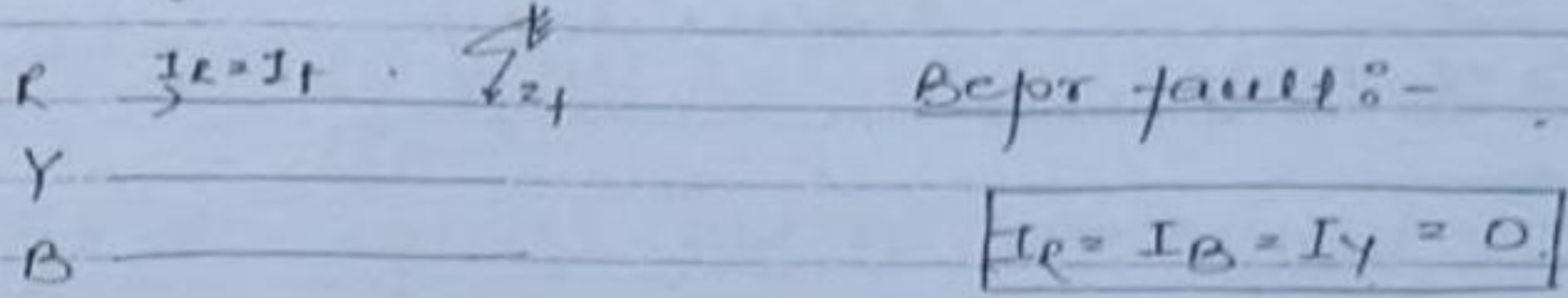

During fault:

$$I_R = I_f$$

$$I_Y = I_B = 0$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_f \\ 0 \\ 0 \end{bmatrix}$$

$$I_{R0} = \frac{1}{3} I_f = I_{R1} = I_{R2}$$

$$I_{R1} = I_{R2} = I_{R0} = \frac{I_f}{3} = \frac{I_{R0}}{3} \rightarrow \text{①}$$

→ All sequence currents are equal & LG fault.

$$V_R = V_f = I_f Z_f = I_R Z_f = 3 I_{R1} Z_f$$

$$V_{R1} + V_{R2} + V_{R0} = 3 I_{R1} Z_f$$

substituting values of V

$$\rightarrow (E - I_{R1} Z_1) - I_{R2} Z_2 - I_{R0} Z_0 = 3 I_{R1} Z_f$$

Current are equal.

$$\rightarrow E - I_{R1} Z_1 - I_{R1} Z_2 - I_{R1} Z_0 = 3 I_{R1} Z_f$$


$$I_f = \frac{E}{Z_1 + Z_2 + Z_0 + 3Z_f} = I_{R_2} = I_{R_0} \quad \text{--- (2)}$$

$$I_{fLG} = I_f = 3I_{R_1}$$

$$\therefore I_{fLG} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_f}$$

Objective :-

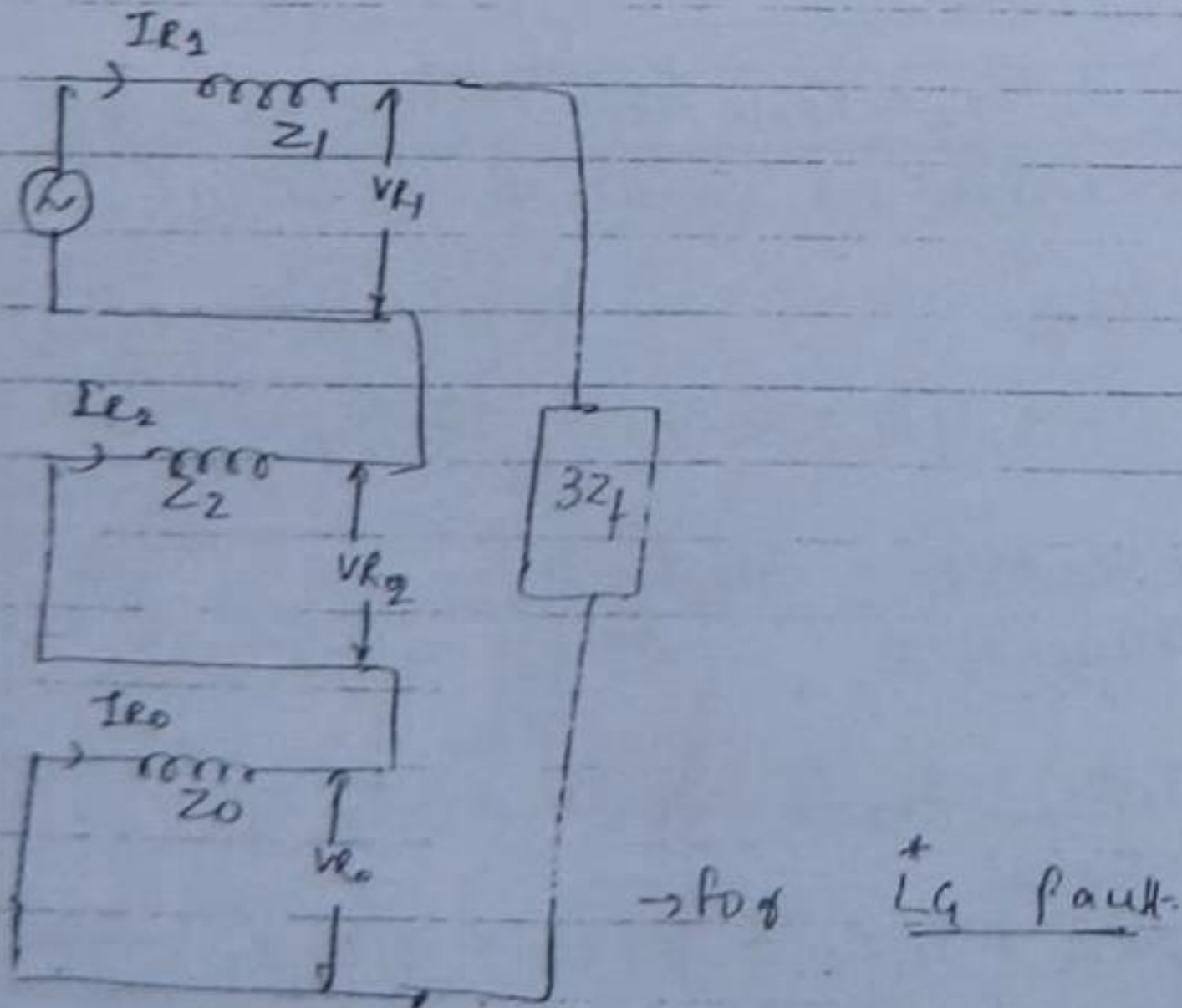→ Particular fault for all sequence current equal → LG fault.



& Comments


for LG fault :-

→ All sequence n/w are connected in series

→ All sequence currents are equal.

$$\rightarrow I_{fLG} = 3I_{R1} = 3I_{E2} = 3I_{R0} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_f}$$

line to line fault :-

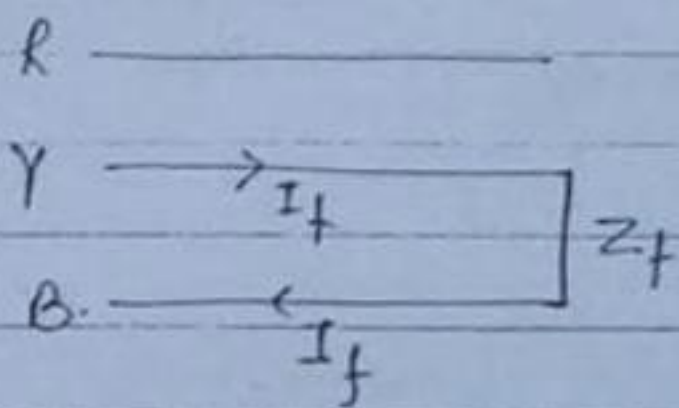


Before fault


$$I_R = I_Y = I_B = 0$$

During fault :-

$$I_f = I_Y = -I_B$$

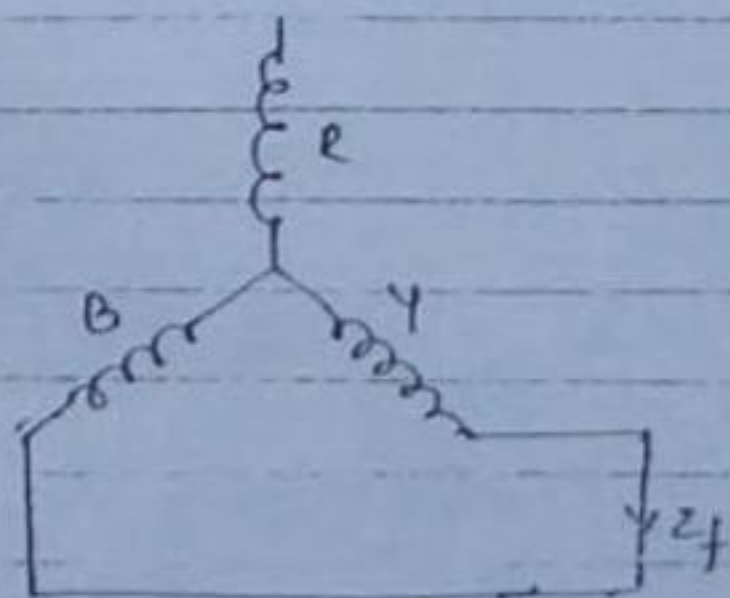

(Current circulates as shown)

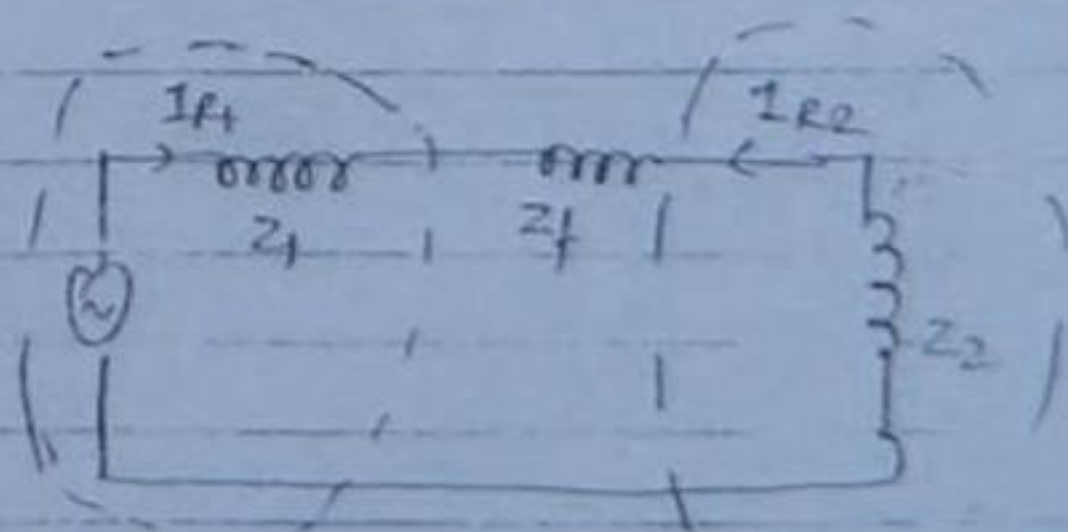

→ Fault in which fault current is $\sqrt{3} I_{R1}$ or $\sqrt{3} I_{R2} \rightarrow LL$ fault.

$$I_{R1} = -I_{R2} \quad \& \quad I_{R0} = 0$$

Two sequences are connected in series opposition

Magnitude :-

$$I_{R1} = -I_{R2} = \frac{E}{Z_1 + Z_2 + Z_f}$$

Calculating I_f

$$I_{fLL} = I_f = I_{R0} + a^2 I_{R1} + a I_{R2}$$
$$= (a^2 - a) I_{R1}$$

$$\therefore (a^2 - a) = (-0.5 - j0.866 + 0.5 - j0.866)$$
$$= -j1.732 = -j\sqrt{3}$$

$$I_{fLL} = \frac{-j\sqrt{3}E}{Z_1 + Z_2 + Z_f}$$

$$|I_{fLL}|^2 = \frac{\sqrt{3}E}{Z_1 + Z_2 + Z_f}$$

Comments:

for line to line fault :-


→ Positive and negative sequence n/w are connected in series opposition.

→ $I_{R1} = -I_{R2}$ and $I_R = 0$

→ Magnitude of fault current is


$$I_{fLL} = \sqrt{3} I_d R_1 = \sqrt{3} I_d R_2 = \frac{\sqrt{3} E}{Z_1 + Z_2 + Z_f}$$

Double line ground fault:

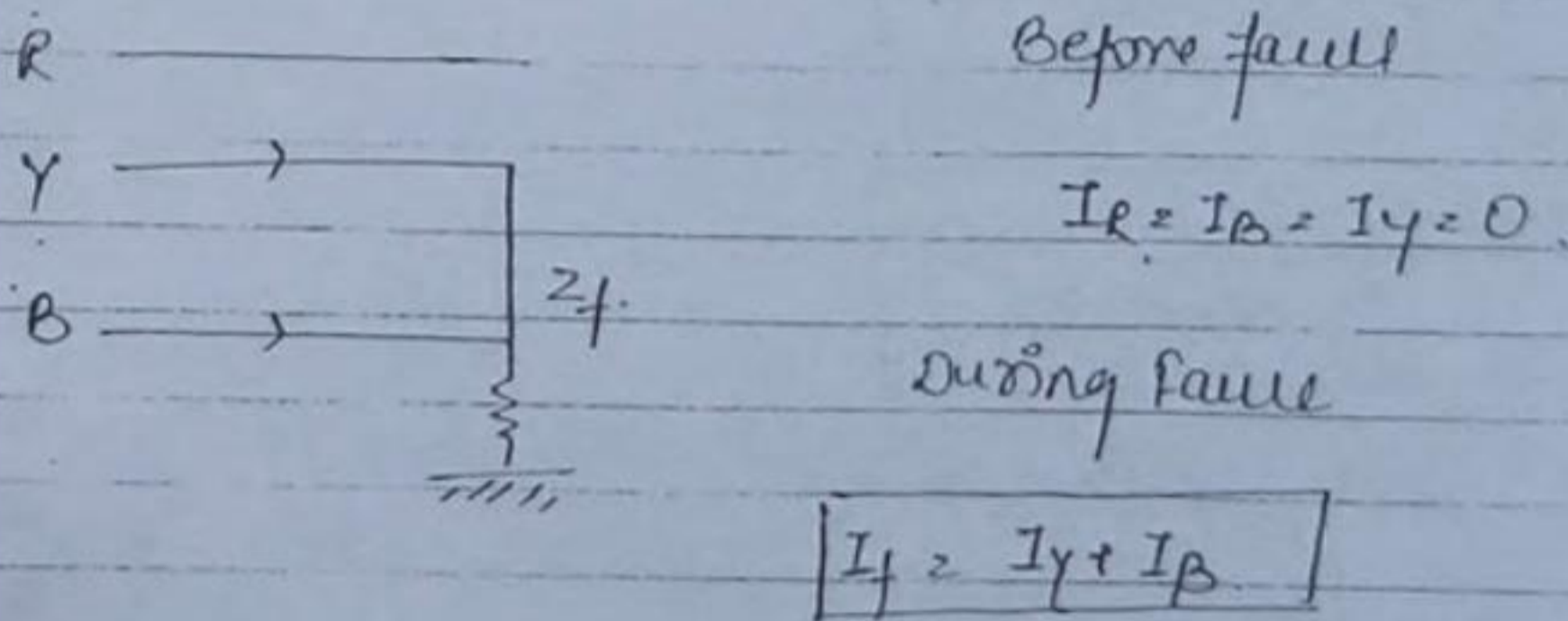

Derivation:

$$V_f = V_Y = V_B = I_f Z_f$$

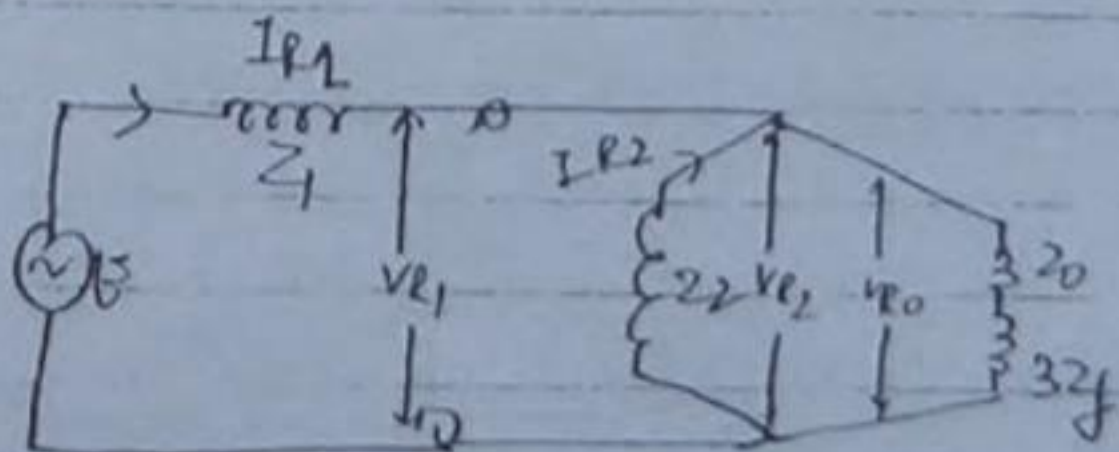

All sequences are in parallel. so

$$\rightarrow \boxed{V_{R1} = V_{R2} = V_{R0}}$$

$$\boxed{I_{R1} = -(I_{R2} + I_{R0})} \rightarrow \text{objective}$$

Magnitude:

$$\boxed{I_{R1} = \frac{E}{Z_1 + (Z_2 \parallel (Z_0 + 3Z_f))}}$$

$$\nabla \boxed{I_{R2} = -I_{R1} \times \frac{Z_0 + 3Z_f}{Z_2 + Z_0 + 3Z_f}}$$

$$\boxed{I_{R0} = -I_{R1} \times \frac{Z_2}{Z_2 + Z_0 + 3Z_f}}$$

using sequence currents find I_f and I_B .

$I_{f/2}$

$$\boxed{I_f = I_f + I_B}$$

$I_{f/2}$

Magnitude of double line fault is 3 times the zero fault!

$I_{R=0}$

$$\overline{I_{R1} + I_{R2} + I_{R0} = 0}$$

$$I_{f_{LLG}} = I_A + I_B$$

$$= (I_{R0} + a^2 I_{R1} + a I_{R2}) + (I_{R0} + a I_{R1} + a^2 I_{R2})$$

$$I_{f_{LLG}} = [2I_{R0} + (a^2 + a)I_{R1} + (a^2 + a)I_{R2}]$$

$$I_{f_{LLG}} = 2I_{R0} - I_{R1} - I_{R2}$$

$$\because a^2 + a = -1$$

$$2I_{R0} - (I_{R1} + I_{R2})$$

**

$$I_{f_{LLG}} = 3I_{R0}$$

$$\because I_{R1} + I_{R2} = -I_{R0}$$

Problem:-

So a balanced 3- ϕ /s/m.

Comment:-

→ All sequence n/w are connected in parallel.


→ $V_{R1} = V_{R2} = V_{R0}$.

→ $I_{R1} = -(I_{R2} + I_{R0})$

Problem:-

The current in each phase of a balanced 3 ϕ system is 10 A. The phase sequence is RYB. Find the resultant sequence current.

Solution:-

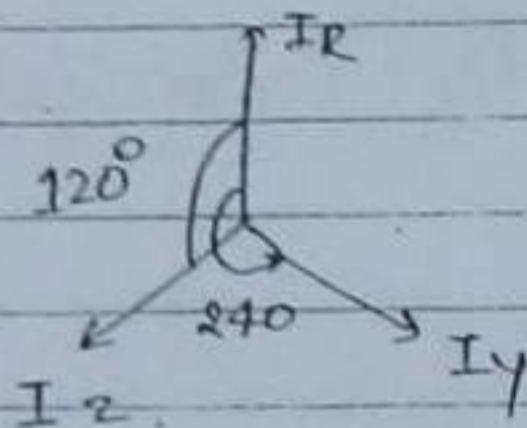

$$I_R = 10 \angle 0^\circ = 10$$

$$I_Y = 10 \angle 240^\circ = a^2 10$$

$$I_B = 10 \angle 120^\circ = a 10$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} 10 \\ 10a^2 \\ 10a \end{bmatrix}$$

$$I_{R0} = \frac{1}{3} [10 + 10a^2 + 10a] = \frac{10}{3} \times 0 = 0 \text{ A}$$

$$I_{R1} = \frac{1}{3} [10 + 10a^3 + 10a^3] = \frac{1}{3} \times 30 = 10 \text{ A}$$

$$I_{R2} = \frac{1}{3} [10 + 10a^3 + 10a^3] = \frac{1}{3} [10 + 10a + 10a^2] = 0 \text{ A}$$

Problem 2:

In above c/m the fuses in Y and B phase are removed.


$$I_Y = I_B = 0, \quad I_R = 10$$

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix}$$

$$I_{R0} = I_{R1} = I_{R2} = 10/3$$

* Under balanced condition we only have +ve sequence cur

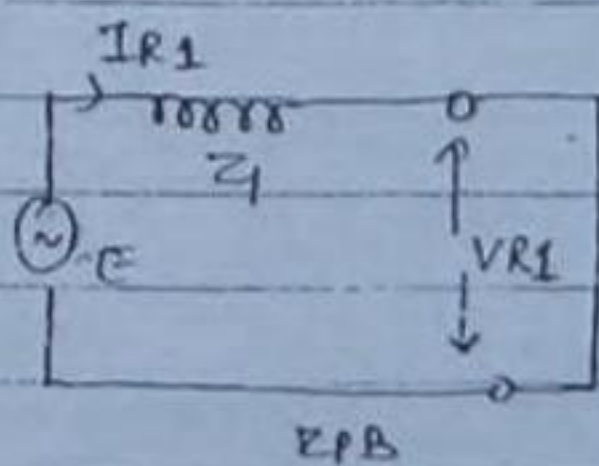3-φ fault using sequence N/W (+ve sequence):



$$\begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ I_{R1} \\ 0 \end{bmatrix}$$

$$\boxed{I_{f, 3\phi} = I_{R1} = E/Z_1}$$

$$I_R = I_{R1}$$

$$I_Y = a^2 I_{R1}$$

$$I_B = a I_{R1}$$

→ In phase fault the fault ~~impedance~~ ^{current} will not is not

not limited by impedance Z_f , hence Z_f is not considered in 3 ϕ fault.

→ Ground also do not effect the 3 ϕ fault current.
Also no difference b/w 3 ϕ fault and ground fault.

→ All the 3 ϕ voltage including the sequence voltage is zero.

Comparison:


3- ϕ fault

$$I_{f-3\phi} = \frac{E}{Z_1}; Z_f = 0$$

Line to Ground fault

$$\rightarrow I_{fLG} = \frac{3E}{Z_1 + Z_2 + Z_0}$$

Case: 1 Solidly grounded alternator:

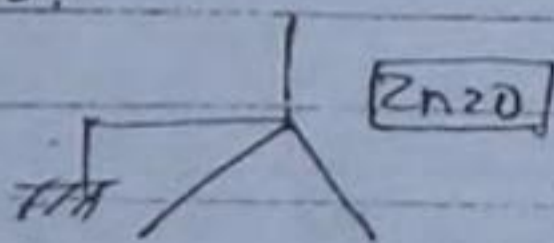

$$Z_0 = Z_{a0} + 3Z_n$$

$$= Z_{a0}$$

∴ 4 alternate sequence current

$$Z_2 \approx Z_1$$

$$Z_0 \gg Z_1$$

$$I_{f3\phi} = \frac{E}{Z_1} \text{ --- (1)}$$

$$I_{fLG} = \frac{3E}{Z_1 + (\approx Z_1) + (< Z_1)}$$


$$= \frac{3E}{2Z_1} \approx 1.5 \times \frac{E}{Z_1}$$

$$\boxed{I_{fLG} > I_{f3\phi}}$$

$$= \boxed{1.5 \times I_{f3\phi}}$$

- For solidly grounded alternator LG fault is severe.

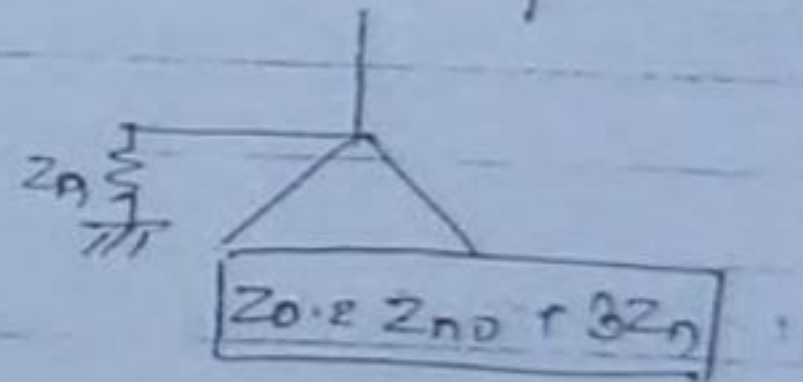Case 2: Alternator neutral grounded with the impedance Z_n



Z_0 depends on Z_n .

$$I_{f3\phi} = \frac{E}{Z_1}$$

$$I_{fLG} = \frac{3E}{Z_1 + Z_0 + Z_{G0} + 3Z_n}$$

Here severity of fault is decided by Z_n

$$\text{If } Z_n = \frac{1}{3}(Z_1 - Z_0)$$

$$\text{then } I_{fLG} = \frac{3E}{Z_1 + (\approx Z_1) + Z_{G0} + 3\left(\frac{1}{3}(Z_1 - Z_0)\right)}$$

$$\approx \frac{3E}{3Z_1} \approx I_{f3\phi}$$

*

$$\boxed{I_{f3\phi} \approx I_{fLG} \quad \text{for } Z_n = \frac{1}{3}(Z_1 - Z_0)}$$

$$\begin{aligned} & \rightarrow < \frac{1}{3}(Z_1 - Z_{00}) ; I_{fLQ} > I_{f3\phi} \\ & \text{I}_{fLQ} > I_{f3\phi} \\ \text{of } Z_0 & \rightarrow = \frac{1}{3}(Z_1 - Z_0) \Rightarrow I_{fLQ} = I_{f3\phi} \\ & \rightarrow > \frac{1}{3}(Z_1 - Z_{00}) \Rightarrow I_{f3\phi} > I_{fLQ} \end{aligned}$$

Objective


① zero sequence current can flow from a line into a x_{mll} bank if the winding of x_{mll} are.

a) $\Delta - \Delta$

b) $\Delta - Y$

c) $Y - Y_1$

d) $\Delta - \Delta$

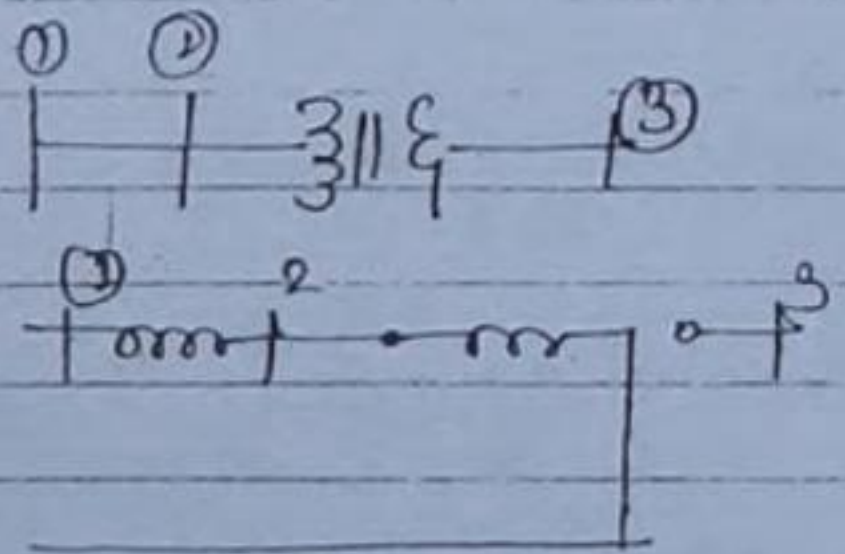


② for s/m shown in figure what is the L-G fault on in right side of x_{mll} equivalent to

a) L-G fault on G/r side of x_{mll}


b) L-L fault on G/r of x_{mll}

c) LL fault on G/r side of x_{mll}

d) 3 ϕ fault on G/r x_{mll}

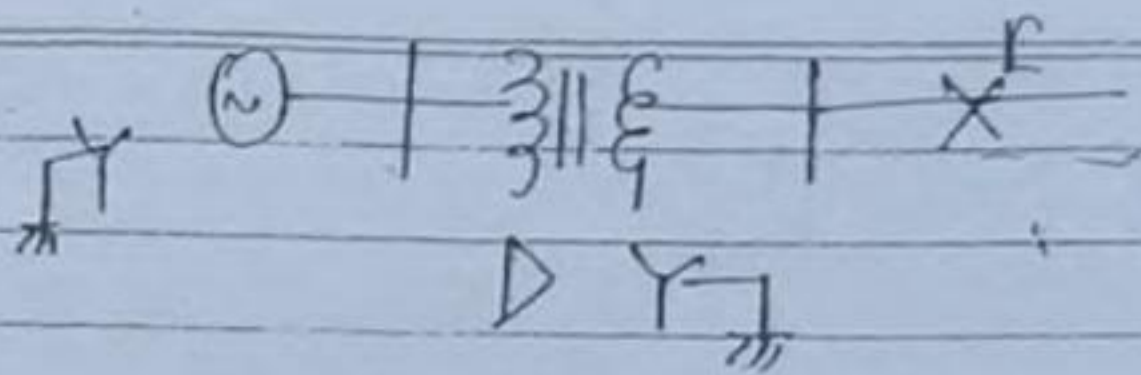

zero sequence diagram.

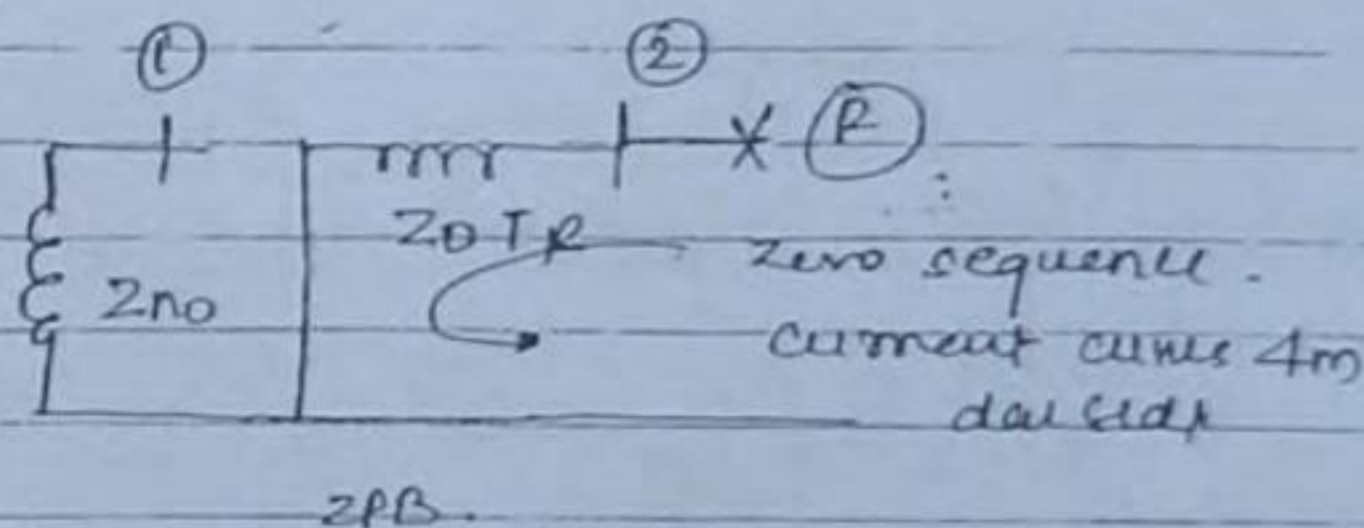

not supplying the zero sequence current so L-L fault on GTR side

③

The L-G fault and the 3φ fault at the terminal of unloaded synchronous GTR is to be same. If terminal voltage is 1 pu, $Z_1 = Z_2 = Z_{12} = j0.1$ and $Z_0 = j0.05$ pu of for the alternator, then the required inductive reactance for nodal grounding is -

$$Z_n = \frac{1}{3} (Z_1 - Z_{G0})$$

$$\frac{1}{3} (j0.1 - 0.05j)$$

$$= 0.0166j$$


$$0.066$$

$$\sqrt{0.05}$$


$$0.01$$

$$0.015$$

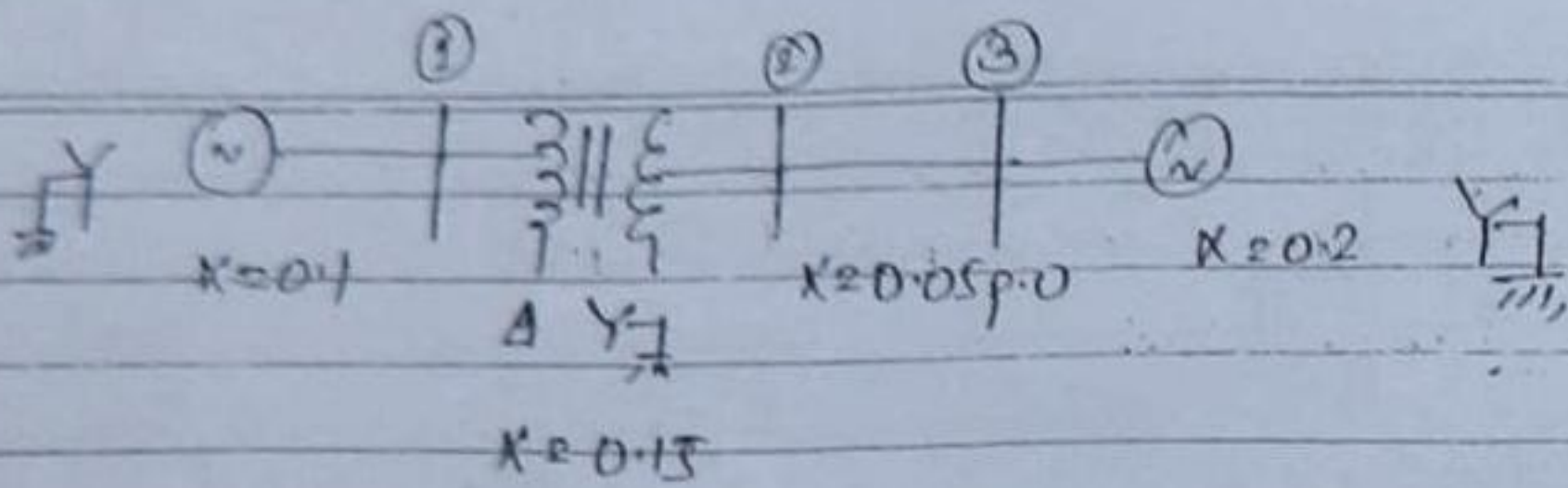④ The zero sequence reactances are indicated in n/w shown below. All the equipment have equal sequence impedences, if L-G fault occurs on bus 3φ the p.2 fault almost is




→ Reducing two sequential reactance :-

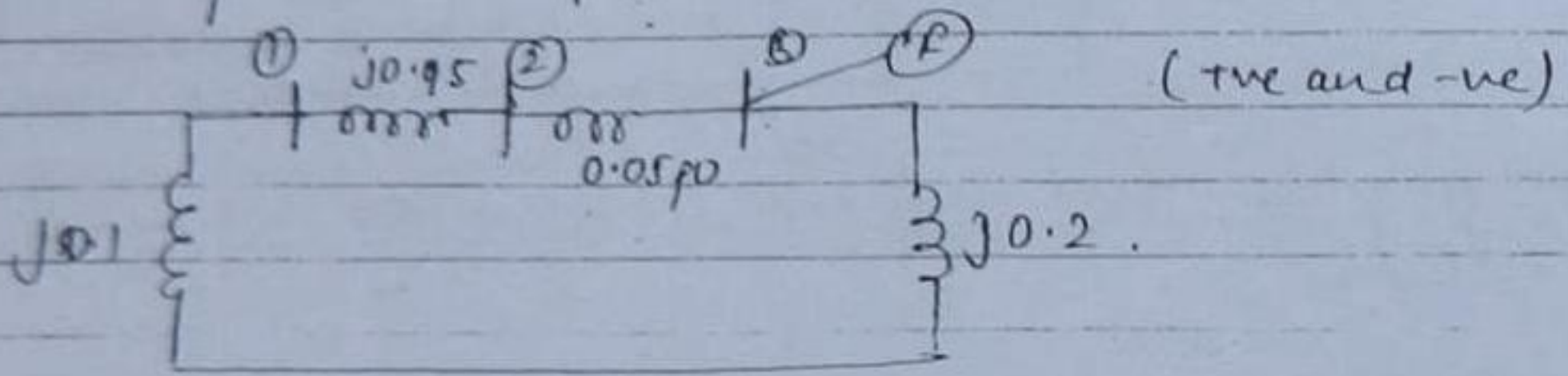

$$\Rightarrow (0.1j + j0.15 + j0.05) \parallel j0.2$$
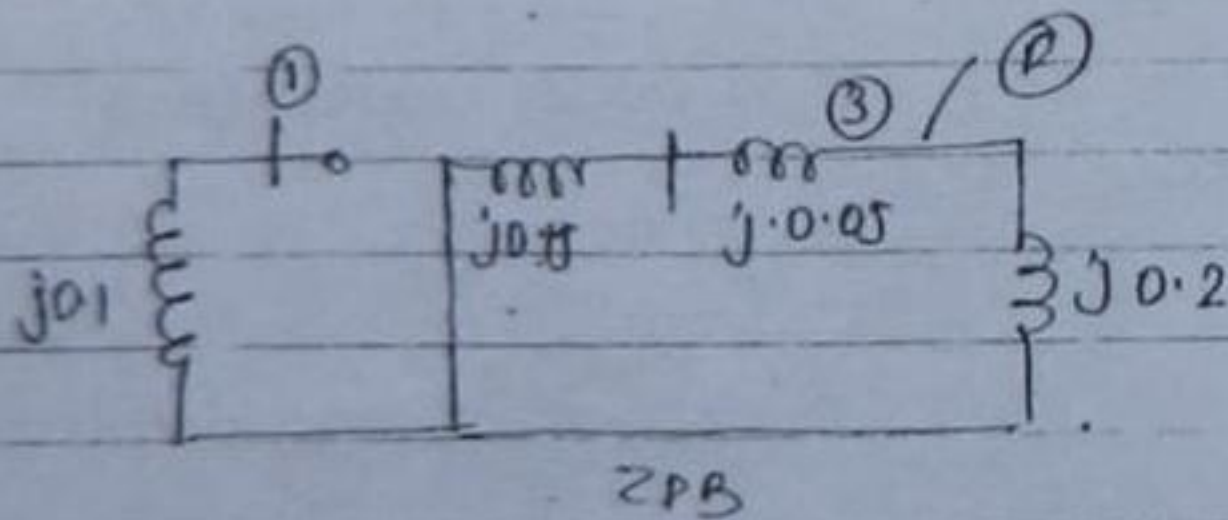
$$= Z_{1TH} = Z_{2TH} = j0.12 \text{ p.u.}$$



$$\Rightarrow (j0.15 + j0.05) \parallel j0.2$$

$$Z_{om} = j0.1 \text{ p.u.}$$

$$\eta = \frac{3E}{Z_1 + Z_2 + Z_0} = \frac{3 \times 1}{j0.12 + j0.12 + j0.1} = 8.823 \angle -90^\circ \text{ p.u.}$$

4. In an unbalanced 3- ϕ s/m the currents are measured as $I_R = 0$, $I_Y = 6 \angle 60^\circ$, $I_B = 6 \angle -120^\circ$. The corresponding sequence currents will be.

a) $0 \quad 3 - j\sqrt{3} \quad -3 + j\sqrt{3}$

b) $0 \quad -3 - j\sqrt{3} \quad 3 - j\sqrt{3}$

c) $0 \quad -9 + j\sqrt{3} \quad 9 - j3\sqrt{3}$

d) $0 \quad 9 - j\sqrt{3} \quad -9 + j3\sqrt{3}$

$$\begin{bmatrix} I_{R_0} \\ I_{R_1} \\ I_{R_2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ 6 \angle 60^\circ \\ 6 \angle -120^\circ \end{bmatrix}$$

$$I_{R_0} = \frac{1}{3} [0 + 6 \angle 0^\circ + 6 \angle -120^\circ]$$

$$I_{R_1} = \frac{1}{3} [0 + a^2 6 \angle 60^\circ + a 6 \angle -120^\circ]$$

$$I_{R_2} = \frac{1}{3} [0 + a 6 \angle 60^\circ + a^2 6 \angle -120^\circ]$$

5) A star connect 3 ϕ , 11KV, 25MVA alternator with its neutral grounded with 0.33 pu reactance and Z_1, Z_2 and Z_0 reactances of 0.2, 0.1, 0.1 respectively. A SLG fault on one of its terminals would result a fault MVA of

2) $0.033 \times 25 = 0.825$

a) 150 MVA

b) 125 MVA

c) 100 MVA

d) 50 MVA

$$I_{sc} = I \times \frac{100}{\%Z}$$

$$\frac{I}{I_{sc}} = Z_{pu}$$

$$I_{sc} = \frac{1}{Z_{pu}}$$

$$I_{FLG} = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_n} = \frac{3 \times 11 \times 10^3}{0.2 + 0.1 + 0.1 + 3 \times 0.33} = j6 \text{ pu}$$

$$\therefore I_{FLG} = 6 \text{ pu}$$

$$\text{Since MVA} = 6 \text{ pu}$$

$$\text{Base MVA} = 25 \text{ MVA}$$

$$\text{Since MVA} = 6 \times 25 = 150 \text{ MVA}$$