

Printed pages:2

Sub Code:NEE502

Paper Id:

2	0	3	2
---	---	---	---

Roll No:

--	--	--	--	--	--	--	--	--	--

B TECH**(SEM 5) THEORY EXAMINATION 2017-18****POWER ELECTRONICS****Time: 3 Hours****Total Marks: 100****Note:** (i) Attempt all questions. If required any missing data; then choose suitably.

(ii) All questions carry equal marks.

SECTION -A

1. Attempt all question in brief. (2x10=20)
- Draw transfer characteristic of MOSFET.
 - What are the advantage and disadvantage of on-off control?
 - What are the advantage and disadvantage of phase angle control?
 - What is a cycloconverter?
 - What are the advantage and disadvantage of cycloconverter?
 - What is meant by step-up and step-down chopper?
 - What are the advantages of GTO over SCR?
 - What do you mean by holding current and latching current?
 - What are the applications of dc chopper?
 - What are the advantages of single phase bridge converter over single phase mid-point converter?

SECTION -B

2. Attempt any **three** parts of the following (10x3=30)
- Draw the two transistor model of SCR and derive an expression for anode current.
 - Write the applications of power electronics devices.
 - What is the need of protective device in power electronics devices? Explain the snubber circuit with the help of circuit diagram?
 - Explain the construction and working principle of SCR. Also draw the V-I characteristics of SCR.
 - Explain the working principle of single phase to single phase cycloconverter with appropriate Waveform and bridge circuit?

SECTION -C

3. Attempt any **one** part of the following (10x1 =10)
- a) Describe the principle of step-up chopper. Derive an expression for the average output voltage in terms of input dc voltage & duty cycle.
 - b) Draw and explain output characteristic of power MOSFET.
4. Attempt any **one** part of the following (10x1 =10)
- a) A step up chopper has input voltage 220 V and output voltage 660 V. If off time of chopper is 100 micro second, find chopping frequency.
 - b) What does ac voltage controller mean? What are the applications of ac voltage controllers?
5. Attempt any **one** part of the following (10x1 =10)
- a) Explain working of TRIAC.
 - b) Explain working of GTO.
6. Attempt any **one** part of the following (10x1 =10)
- a) Explain single phase transformer connection changer. Draw waveform for input and output voltage.
 - b) Explain single phase to single phase cycloconverter and draw circuit and waveform for resistive load.
7. Attempt any **one** part of the following (10x1 =10)
- a) Explain three phase to single phase cycloconverter with neat diagram
 - b) Explain operation of three phase bridge inverter..