

Printed Pages: 02

Subject Code: NEE502

Paper Id: 120516

Roll No:

--	--	--	--	--	--	--	--	--	--

B TECH
(SEM V) THEORY EXAMINATION 2018-19
POWER ELECTRONICS

Time: 3 Hours

Total Marks: 100

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt all questions in brief.

2 x 10 = 20

- a. What is the function of power modulator?
- b. Give the comparison between transistor and thyristor.
- c. What are the problems associated with firing of parallel connected SCRs?
- d. What are the merits and demerits of load commutated chopper?
- e. Explain freewheeling diode and its effect.
- f. What are the points should be considered while selecting converter?
- g. Explain why the single phase a.c. regulator using two SCRs must have its trigger source isolated from each other.
- h. Discuss the important factors to be considered while feeding transformers through a.c. regulators.
- i. What do you mean by total harmonic distortion of an inverter?
- j. Explain the function of feedback diodes used in antiparallel with transistors in inverters.

SECTION B

2. Attempt any three of the following:

10 x 3 = 30

- a. Draw and explain the turn off characteristic of the SCR. Explain method of turning off an SCR.
- b. Draw and explain the simultaneous triggering circuit of series connected SCRs.
- c. A three phase, half wave converter is supplying a load with a continuous current of 40A over a firing angle from 0 to 75°. What will be the power dissipated by the load at these limiting values of firing angle? The supply voltage is 415V(line).
- d. Derive an expression for the output current in terms of source voltage, load impedance and firing angle for a single phase a.c. voltage controller with RL load.
- e. Briefly explain bipolar and unipolar PWM full bridge inverters.

SECTION C

3. Attempt any one part of the following:

10 x 1 = 10

- (a) Explain the various types of triggering methods of SCR briefly. Which is the universal method and why?
- (b) Describe the turn off process in a GTO with the help of appropriate voltage and current waveforms.

4. Attempt any one part of the following:

10 x 1 = 10

- (a) Explain the continuous conduction mode and non-continuous conduction mode of class A chopper and derive the relation for average load current.
- (b) A d.c. on-off chopper operating at 1kHz and duty cycle of 10% is supplied from a 200 V source. If the load inductance is 10mH and resistance 10Ω. Compute the maximum and minimum current in the load.

5. Attempt any one part of the following:

10 x 1 = 10

- (a) Explain the operation of three phase half wave controlled converter with resistive load, and inductive load. Sketch the associated waveforms also.
- (b) Derive an expression for the output voltage of a three phase fully controlled bridge converter by conducting the following factors: (i) overlap – angle
(ii) source - inductance

6. Attempt any one part of the following:

10 x 1 = 10

- (a) A single phase load of resistance $12\ \Omega$ in series with an inductance of 24 mH is fed from a 240 V , 50 Hz supply by a pair of inverse parallel thyristors. Find the mean power in the load at firing angle of (a) 0° (b) 90° and (c) 120° .Ignore source inductance and device voltage drop
- (b) Describe the basic principle of working of a single phase to single phase cycloconverter for both continuous and discontinuous conductions for a bridge type cycloconverter.

7. Attempt any one part of the following:

10 x 1 = 10

- (a) A single phase bridge inverter delivers power to a series connected RLC load with $R= 2\ \Omega$ and $\omega L= 10\ \Omega$. The period time T is 0.1ms. What value of capacitor C should be load have in order to obtain load commutation for the SCRs. The thyristor turn off time is $10\mu s$. Assume circuit turnoff time $T_{off}= 1.5\ t_q$. Also assume that the load current contains only fundamental components.
- (b) Explain three phase inverter in 180° conduction mode with resistive load, also draw its voltage waveform.